

**SYNERGY SCHOOL  
OF  
ENGINEERING,(SSE)  
DHENKANAL**




**POWER ELECTRONICS  
AND PLC  
(THEORY-5)**

# Chapter-1: Power Semiconductor devices

## Power Diode

### Explain the operation, construction & application of Power Diode

Power Diodes of largest power rating are required to conduct several kilo amps of current in the forward direction with very little power loss while blocking several kilo volts in the reverse direction. Large blocking voltage requires wide depletion layer in order to restrict the maximum electric field strength below the -impact ionization level. Space charge density in the depletion layer should also be low in order to yield a wide depletion layer for a given maximum Electric fields strength. These two requirements will be satisfied in a lightly doped p-n junction diode of sufficient width to accommodate the required depletion layer. Such a construction, however, will result in a device with high resistivity in the forward direction. Consequently, the power loss at the required rated current will be unacceptably high. On the other hand if forward resistance (and hence power loss) is reduced by increasing the doping level, reverse break down voltage will reduce. This apparent contradiction in the requirements of a power diode is resolved by introducing a lightly doped -drift layer of required thickness between two heavily doped p and n layers as shown in Fig 1 (c). Fig 1 (a) and (b) shows the circuit symbol and the photograph of a typical power diode respectively.

   

**Fig.1: Diagram of a power; (a) circuit symbol (b) photograph; (c) schematic cross**

To arrive at the structure shown in Fig 1 (c) a lightly doped **n** epitaxial layer of specified width (depending on the required break down voltage) and donor atom density ( $N$ ) is grown on a heavily doped **n+** substrate ( $N_d \approx 10^{19}$  donor atoms.  $\text{cm}^{-3}$ ) which acts as the cathode. Finally the **p-n** junction is formed by defusing a heavily doped ( $N_a \approx 10^{19}$  acceptor atoms.  $\text{cm}^{-3}$ ) **p+** region into the epitaxial layer. This **p** type region acts as the anode.

The different applications of Power Diode are in SMPs, Snubber, Chopper and freewheeling diode etc.

### Explain V-I characteristics curve of Power Diode

Power Diodes take finite time to make transition from reverse bias to forward bias condition (switch ON) and vice versa (switch OFF). Behavior of the diode current and voltage during these switching periods are important due to the following reasons.

- i) Severe over voltage / over current may be caused by a diode switching at different points in the circuit using the diode.
- ii) Voltage and current exist simultaneously during switching operation of a diode. Therefore, every switching of the diode is associated with some energy loss. At high switching frequency this may contribute significantly to the overall power loss in the diode.

**Observed Turn ON behavior of a power Diode:** Diodes are often used in circuits with  $di/dt$  limiting inductors. The rate of rise of the forward current through the diode during Turn ON has significant effect on the forward voltage drop characteristics. A typical turn on transient is shown in Fig. 2


 


Fig. 2 : Forward current and voltage waveforms of a power diode during Turn On operation.

It is observed that the forward diode voltage during turn ON may transiently reach a significantly higher value  $V_{fr}$  compared to the steady state voltage drop at the steady current  $I_F$ .  $V_{fr}$  (called forward recovery voltage) is given as a function of the forward  $di/dt$  in the manufacturer's data sheet. Typical values lie within the range of 10-30V. Forward recovery time ( $t_{fr}$ ) is typically within 10  $\mu$ s.

**Observed Turn OFF behavior of a Power Diode:** Figure 3 shows a typical turn off behavior of a power diode assuming controlled rate of decrease of the forward current.

 

**Fig. 3: Reverse Recovery characteristics of a power diode**

*Salient features of this characteristic are:*

The diode current does not stop at zero, instead it grows in the negative direction to  $I_{rr}$  called -peak reverse recovery current which can be comparable to  $I_F$ . In many power electronic circuits (e.g. choppers, inverters) this reverse current flows through the main power switch in addition to the load current. Therefore, this reverse recovery current has to be accounted for while selecting the main switch.

Voltage drop across the diode does not change appreciably from its steady state value till the diode current reaches reverse recovery level. In many power electric circuits (choppers, inverters) this may create an effective short circuit across the supply, current being limited only by the stray wiring inductance. Also in high frequency switching circuits (e.g, SMPS) if the time period  $t_4$  is comparable to switching cycle qualitative modification to the circuit behavior is possible.


Towards the end of the reverse recovery period if the reverse current falls too sharply, (low value of  $S$ ), stray circuit inductance may cause dangerous over voltage ( $V_{rr}$ ) across the device. It may be required to protect the diode using an RC snubber.

During the period  $t_5$  large current and voltage exist simultaneously in the device. At high switching frequency this may result in considerable increase in the total power loss.

## SCR

### Layer diagram of SCR and operation & construction of SCR.

Thyristors (also known as the Silicon Controlled Rectifiers or SCRs)

 

**Fig. 4.1: Constructional features of a thyristor**

**(a) Circuit Symbol, (b) Schematic Construction, (c) Photograph**


As shown in Fig 4.1 (b) the primary crystal is of lightly doped **n** type on either side of which two **p** type layers with doping levels higher by two orders of magnitude are grown. As in the case of power diodes and transistors, depletion layer spreads mainly into the lightly doped **n** region. The thickness of this layer is therefore determined by the required blocking voltage of the device. However, due to conductivity modulation by carriers from the heavily doped **p** regions on both side during ON condition the  $-ON$  state voltage drop is less. The outer **n** layers are formed with doping levels higher than both the **p** type layers. The top **p** layer acts as the  $-Anode$  terminal while the bottom **n** layers act as the  $-Cathode$ . The  $-Gate$  terminal connections are made to the bottom **p** layer.

For better switching performance it is required to maximize the peripheral contact area of the gate and the cathode regions. Therefore, the cathode regions are finely distributed between gate contacts of the **p** type layer. An  $-Involuted$  structure for both the gate and the cathode regions is a preferred design structure.

## Explain the two transistor analogy of SCR

### Basic operating principle of a thyristor

The underlying operating principle of a thyristor is best understood in terms of the two transistor analogy as explained below.

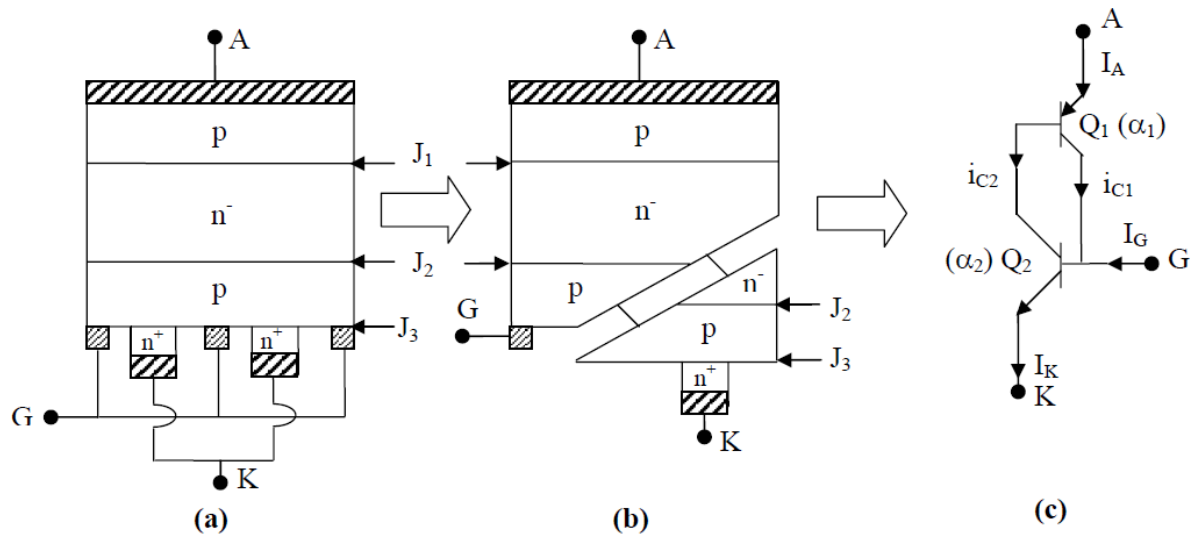

**Fig. 4.2: Two transistor analogy of a thyristor construction.**

(a) Schematic Construction, (b) Schematic division in component transistor

(c) Equivalent circuit in terms of two transistors.

a) Schematic construction,

b) Schematic division in component transistor

c) Equivalent circuit in terms of two transistors.

Let us consider the behavior of this p n p n device with forward voltage applied, i.e. anode positive with respect to the cathode and the gate terminal open. With this voltage polarity J<sub>1</sub> & J<sub>3</sub> are forward biased while J<sub>2</sub> reverse biased.

Under this condition.

$$i_{c1} = \alpha_1 I_A + I_{co1} \quad (4.1)$$

$$i_{c2} = \alpha_2 I_K + I_{co2} \quad (4.2)$$

Where  $\alpha_1$  &  $\alpha_2$  are current gains of Q<sub>1</sub> & Q<sub>2</sub> respectively while I<sub>co1</sub> & I<sub>co2</sub> are reverse



Now from Fig 4.2 (c).

$$i_{c1} + i_{c2} = I_A \quad (4.3)$$

$$\& I_A = I_K \quad (4.4) \quad (\because I_G = 0)$$

Combining Eq 4.1 & 4.4

$$I_A = \frac{I_{co1} + I_{co2}}{1 - (\alpha_1 + \alpha_2)} = \frac{I_{co}}{1 - (\alpha_1 + \alpha_2)} \quad (4.5)$$

Where  $I_{co} \triangleq I_{co1} + I_{co2}$  is the total reverse leakage current of  $J_2$

Now as long as  $V_{AK}$  is small  $I_{co}$  is very low and both  $a_1$  &  $a_2$  are much lower than unity. Therefore, total anode current  $I_A$  is only slightly greater than  $I_{co}$ . However, as  $V_{AK}$  is increased up to the avalanche break down voltage of  $J_2$ ,  $I_{co}$  starts increasing rapidly due to

avalanche multiplication process. As  $I_{co}$  increases both  $a_1$  &  $a_2$  increase and  $a_1 + a_2$  approaches unity. Under this condition large anode current starts flowing, restricted only by the external load resistance. However, voltage drop in the external resistance causes a collapse of voltage across the thyristor. The CB junctions of both  $Q_1$  &  $Q_2$  become forward biased and the total voltage drop across the device settles down to approximately equivalent to a diode drop. The thyristor is said to be in —ON state.

Just after turn ON if  $I_a$  is larger than a specified current called the Latching Current  $I_L$ ,

$a_1$  and  $a_2$  remain high enough to keep the thyristor in ON state. The only way the thyristor can be turned OFF is by bringing  $I_A$  below a specified current called the holding current ( $I_H$ ) where upon  $a_1$  &  $a_2$  starts reducing. The thyristor can regain forward blocking capacity once excess stored charge at  $J_2$  is removed by application of a reverse voltage across A & K (ie, K positive with respect A).

It is possible to turn ON a thyristor by application of a positive gate current (flowing from gate to cathode) without increasing the forward voltage across the device up to the forward break-over level. With a positive gate current equation 4.4 can be written as

$$I_K = I_A + I_G \quad (4.6)$$

$$\text{Combining with Eqns. 4.1 to 4.3} \quad I_A = \frac{\alpha_2 I_G + I_{co}}{1 - (\alpha_1 + \alpha_2)} \quad (4.7)$$

Obviously with sufficiently large  $I_G$  the thyristor can be turned on for any value of  $I_{co}$  (and hence  $V_{AK}$ ). This is called gate assisted turn on of a Thyristor. This is the usual method by which a thyristor is turned ON.

When a reverse voltage is applied across a thyristor (i.e, cathode positive with respect to anode.) junctions  $J_1$  and  $J_3$  are reverse biased while  $J_2$  is forward biased. Of these, the junction  $J_3$  has a very low reverse break down voltage since both the  $n^+$  and  $p$  regions on either side of this junction are heavily doped. Therefore, the applied reverse voltage is almost entirely supported by junction  $J_1$ . The maximum value of the reverse voltage is restricted by

a) The maximum field strength at junction  $J_1$  (avalanche break down)


b) Punch through of the lightly doped  $n^-$  layer.

Since the  $p$  layers on either side of the  $n^-$  region have almost equal doping levels the avalanche break down voltage of  $J_1$  &  $J_2$  are almost same. Therefore, the forward and the reverse break down voltage of a thyristor are almost equal. Up to the break down voltage of  $J_1$  the reverse current of the thyristor remains practically constant and increases sharply after this voltage. Thus, the reverse characteristics of a thyristor is similar to that of a single diode.

If a positive gate current is applied during reverse bias condition, the junction  $J_3$  becomes forward biased. In fact, the transistors  $Q_1$  &  $Q_2$  now work in the reverse direction with the roles of their respective emitters and collectors interchanged. However, the reverse  $\alpha_1$  &  $\alpha_2$  being significantly smaller than their forward counterparts latching of the thyristor does not occur. However, reverse leakage current of the thyristor increases considerably increasing the OFF state power loss of the device.

If a forward voltage is suddenly applied across a reverse biased thyristor, there will be considerable redistribution of charges across all three junctions. The resulting current can become large enough to satisfy the condition  $\alpha_1 + \alpha_2 = 1$  and consequently turn on the thyristor. This is called dvdt turn on of a thyristor and should be avoided.

## Static V-I characteristics & Dynamic characteristics of SCR.

 

**Fig. 4.3: Static output characteristics of a Thyristor**

The circuit symbol in the left hand side inset defines the polarity conventions of the variables used in this figure.

With  $i_g = 0$ ,  $V_{AK}$  has to increase up to forward break over voltage  $V_{BRF}$  before significant anode current starts flowing. However, at  $V_{BRF}$  forward break over takes place and the voltage across the thyristor drops to  $V_H$  (holding voltage). Beyond this point voltage across the thyristor ( $V_{AK}$ ) remains almost constant at  $V_H$  (1-1.5v) while the anode current is determined by the external load.

The magnitude of gate current has a very strong effect on the value of the break over voltage as shown in the figure. The right hand side figure in the inset shows a typical plot of the forward break over voltage ( $V_{BRF}$ ) as a function of the gate current ( $I_g$ )


After -Turn ON|| the thyristor is no more affected by the gate current. Hence, any current pulse (of required magnitude) which is longer than the minimum needed for -Turn ON|| is sufficient to effect control. The minimum gate pulse width is decided by the external

circuit and should be long enough to allow the anode current to rise above the latching current ( $I_L$ ) level.

The left hand side of Fig 4.3 shows the reverse i-v characteristics of the thyristor. Once the thyristor is ON the only way to turn it OFF is by bringing the thyristor current below holding current ( $I_H$ ). The gate terminal has no control over the turn OFF process. In ac circuits with resistive load this happens automatically during negative zero crossing of the supply voltage. This is called -natural commutation or -line commutation. However, in dc circuits some arrangement has to be made to ensure this condition. This process is called -forced commutation.

During reverse blocking if  $i_g = 0$  then only reverse saturation current ( $I_s$ ) flows until the reverse voltage reaches reverse break down voltage ( $V_{BRF}$ ). At this point current starts rising sharply. Large reverse voltage and current generates excessive heat and destroys the device. If  $i_g > 0$  during reverse bias condition the reverse saturation current rises as explained in the previous section. This can be avoided by removing the gate current while the thyristor is reverse biased.

The static output i-v characteristics of a thyristor depends strongly on the junction temperature as shown in Fig 4.4.

 

**Fig. 4.4: Effect of junction temperature ( $T_j$ ) on the output i – v characteristics of a thyristor.**


### Dynamic characteristics

Turn-on and turn-off characteristics of an SCR are called the dynamic characteristics of the SCR.
 
#### (a) Turn-On Characteristic.


The turn-on time characteristic shows the variation of current and voltage during turn-on. Turn-on time is defined as the time from the initiation of triggering, when the SCR offers infinite impedance to the flow of anode current, to the time when an equilibrium charge distribution is established throughout the device together with a steady state forward voltage drop. The turn-on time is about 1 to 3 micro seconds for the SCR readily available commercially.

The above Figure shows the form of current rise during the transition from the non-



conducting to the fully conducting state. The time  $t_0$  indicate the initiation of turn-on which is caused by a step function of voltage applied to the gate. The period  $t_d$  is the delay time between the front of the gate pulse and the beginning of a rapid rate of increase of anode current. During the initial interval of turn-on ( $t_d$ ) only a small area near the gate electrode conducts anode current.  $t_d$  is due to the charge build up time and decreases with the increase in

gate current. The rise time,  $t_r$  depends on the speed at which charges build up to support the final anode current,  $I_A$ .  $t_r$  is independent of gate current but depends upon the widths of base construction of SCR. The sum of  $t_d$  and  $t_c$  gives turn-on time  $t_{on}$ . The turn-on time  $t_{on}$  depends on the anode circuit parameters, gate current amplitude and rise time. The turn-on time is important in pulse triggering.

 

### (b) Turn-off Characteristic.

Turn-off means that all forward conduction has ceased and the re-application of a positive voltage to the anode will not cause flow of current without there being a gate signal. The turn-off characteristic is shown in figure. The time  $t_0$  indicates the instant of application of reverse voltage,  $t_{rr}$  is the duration for which the reverse recovery current flows after application of reverse voltage and  $t$  is the time required for the recombination of all excess carriers in the inner two layers of the device. The sum of time duration  $t_{rr}$  and time duration  $t$  gives the turn-off time  $t_{off}$ , that is  $t_{off} = t_{rr} + t_{gr}$ . At the end of turn-off time, a depletion layer gets developed across junction  $J_2$  and now SCR is capable of withstanding forward voltage. The turn-off time depends upon anode current, magnitude of reverse voltage and the rate of application of forward voltage.

## Applications of SCR

### 1. Power Control.

Because of the bistable characteristics of semiconductor devices, whereby they can be switched on and off, and the efficiency of gate control to trigger such devices, the SCRs are ideally suited for many industrial applications. SCRs have got specific advantages over

saturable core reactors and gas tubes owing to their compactness, reliability, low losses, and speedy turn-on and turn-off.

The bistable states (conducting and non-conducting) of the SCR and the property that enables fast transition from one state to the other are made use of in the control of power in both ac and dc circuits.

## **2. Switching.**

Thyristor, being bistable device is widely used for switching of power signals owing to their long life, high operation speed and freedom from other defects associated with mechanical and electro-mechanical switches.

## **3. Zero Voltage Switching.**

In some ac circuits it is necessary to apply the voltage to the load when the instantaneous value of this voltage is going through the zero value. This is to avoid a high rate of increase of current in case of purely resistive loads such as lighting and furnace loads, and thereby reduce the generation of radio noise and hot-spot temperatures in the device carrying the load current.

## **4. Over-Voltage Protection.**

SCRs can be employed for protecting other equipment from over-voltages owing to their fast switching action. The SCR employed for protection is connected in parallel with the load. Whenever the voltage exceeds a specified limit, the gate of the SCR will get energized and trigger the SCR. A large current will be drawn from the supply mains and voltage across the load will be reduced. Two SCRs are used—one for the positive half-cycle and the other for negative half-cycle.

## **5. Pulse Circuits.**

SCRs are used for producing high voltage/current pulses of desired waveform and duration.

## **6. Battery Charging Regulator.**

## DIAC


### Operation, construction of DIAC and V-I characteristics curve

A diac is a two-terminal, three layer bidirectional device which can be switched from its OFF state to ON state for either polarity of applied voltage.

The diac can be constructed in either npn or pnp form. Fig. (i) shows the basic structure of a diac in pnp form. The two leads are connected to p-regions of silicon separated by an n-region. The structure of diac is very much similar to that of a transistor. However, there are several important differences:

- (i) There is no terminal attached to the base layer.
- (ii) The three regions are nearly identical in size.
- (iii) The doping concentrations are identical (unlike a bipolar transistor) to give the device symmetrical properties.

Fig. (ii) shows the symbol of a diac.

 


### Operation

When a positive or negative voltage is applied across the terminals of a diac, only a small leakage current  $I_{BO}$  will flow through the device. As the applied voltage is increased, the leakage current will continue to flow until the voltage reaches the breakover voltage  $V_{BO}$ . At this point, avalanche breakdown of the reverse-biased junction occurs and the device exhibits negative resistance i.e. current through the device increases with the decreasing values of applied voltage. The voltage across the device then drops to 'breakback' voltage  $V_W$ . Fig (iii) shows the V-I characteristics of a diac. For applied positive voltage less than  $+V_{BO}$  and negative voltage less than  $-V_{BO}$ , a small leakage current ( $\pm I_{BO}$ ) flows through the device. Under such conditions, the diac blocks the flow of current and effectively behaves



as an open circuit. The voltages  $+V_{BO}$  and  $-V_{BO}$  are the breakdown voltages and usually have a range of 30 to 50 volts.

 

**Fig (iii) V-I characteristics of a diac**

When the positive or negative applied voltage is equal to or greater than the breakdown voltage, diac begins to conduct and the voltage drop across it becomes a few volts. Conduction then continues until the device current drops below its holding current. Note that the breakover voltage and holding current values are identical for the forward and reverse regions of operation. The DIAC can be used in many applications such as motor speed controls and light dimmers circuit.


### **Applications of DIAC**

The **diacs**, because of their symmetrical bidirectional switching characteristics, are widely used as triggering devices in triac phase control circuits employed for lamp dimmer, heat control, universal motor speed control etc.

Although a **triac** may be fired into the conducting state by a simple resistive triggering circuit, but triggering devices are typically placed in series with the gates of SCRs and triacs as they give reliable and fast triggering. Diac is the most popular triggering device for the triac. This is illustrated in the following applications.
 
### 1. Triac Lamp Dimmer Circuit.


The circuit for a triac controlled by an R-C phase-shift network and a diac is given in figure. This circuit is an example of a simple lamp dimmer. The triac conduction angle is adjusted by adjusting the potentiometer R. The longer the triac conducts, the brighter the lamp will be. The diac acts like an open-circuit until the voltage across the capacitor exceeds its breakover or switching voltage (and the triac's required gate trigger voltage).



*Triac Lamp Dimmer Circuit*
 
### 2. Heat Control Circuit.

A typical diac-triac circuit used for smooth control of ac power to a heater is shown in figure. The capacitor  $C_1$  in series with choke L across the triac slows-up the voltage rise across the device during off-state. The resistor  $R_4$  across the diac ensures smooth control at all positions of potentiometer  $R_2$ . The triac conduction angle is adjusted by adjusting the potentiometer  $R_2$ . The longer the triac conducts, the larger the output will be from the heater. Thus a smooth control of the heat output from the heater is obtained.



(Heat Control Circuit using Diac)

## TRIAC

### Operation, construction of TRIAC and V-I characteristics curve

The Triac is a member of the thyristor family. But unlike a thyristor which conducts only in one direction (from anode to cathode) a triac can conduct in both directions. Thus a triac is similar to two back to back (anti parallel) connected thyristors but with only three terminals.

#### Construction and operating principle

Fig. 5 (a) and (b) show the circuit symbol and schematic cross section of a triac respectively. As the Triac can conduct in both the directions the terms -anode and -cathode are not used for Triacs. The three terminals are marked as MT<sub>1</sub> (Main Terminal 1), MT<sub>2</sub> (Main Terminal 2) and the gate by G. As shown in Fig 5 (b) the gate terminal is near MT<sub>1</sub> and is connected to both

N<sub>3</sub> and P<sub>2</sub> regions by metallic contact. Similarly MT<sub>1</sub> is connected to N<sub>2</sub> and P<sub>2</sub> regions while MT<sub>2</sub> is connected to N<sub>4</sub> and P<sub>1</sub> regions.


 


Fig.5 Circuit symbol and schematic construction of a Triac  
(a) Circuit symbol (b) Schematic construction.

#### V-I characteristics

From a functional point of view a triac is similar to two thyristors connected in anti parallel. Therefore, it is expected that the V-I characteristics of Triac in the 1<sup>st</sup> and 3<sup>rd</sup> quadrant of the V-I plane will be similar to the forward characteristics of a thyristors. As shown in Fig. 6, with no signal to the gate the triac will block both half cycle of the applied ac voltage provided its peak value is lower than the break over voltage ( $V_{BO}$ ) of the device. However, the turning on of the triac can be controlled by applying the gate trigger pulse at the desired

instance. Mode-1 triggering is used in the first quadrant where as Mode-3 triggering is used in the third quadrant.

 

**Fig. 6 : Steady state V – I characteristics of a Triac**

As such, most of the thyristor characteristics apply to the triac (ie, latching and holding current). However, in a triac the two conducting paths (from  $MT_1$  to  $MT_2$  or from  $MT_1$  to  $MT_1$ ) interact with each other in the structure of the triac. Therefore, the voltage, current and frequency ratings of triacs are considerably lower than thyristors. At present triacs with voltage and current ratings of 1200V and 300A (rms) are available. Triacs also have a larger on state voltage drop compared to a thyristor.


### **Modes of operation of TRIAC and mention the preferred modes**

Since a Triac is a bidirectional device and can have its terminals at various combinations of positive and negative voltages, there are four possible electrode potential combinations as given below

1.  $MT_2$  positive with respect to  $MT_1$ , G positive with respect to  $MT_1$
2.  $MT_2$  positive with respect to  $MT_1$ , G negative with respect to  $MT_1$
3.  $MT_2$  negative with respect to  $MT_1$ , G negative with respect to  $MT_1$
4.  $MT_2$  negative with respect to  $MT_1$ , G positive with respect to  $MT_1$

The triggering sensitivity is highest with the combinations 1 and 3 and are generally used. However, for bidirectional control and uniform gate trigger mode sometimes trigger

modes 2 and 3 are used. Trigger mode 4 is usually avoided. Fig 7 (a) and (b) explain the conduction mechanism of a triac in trigger modes 1 & 3 respectively.

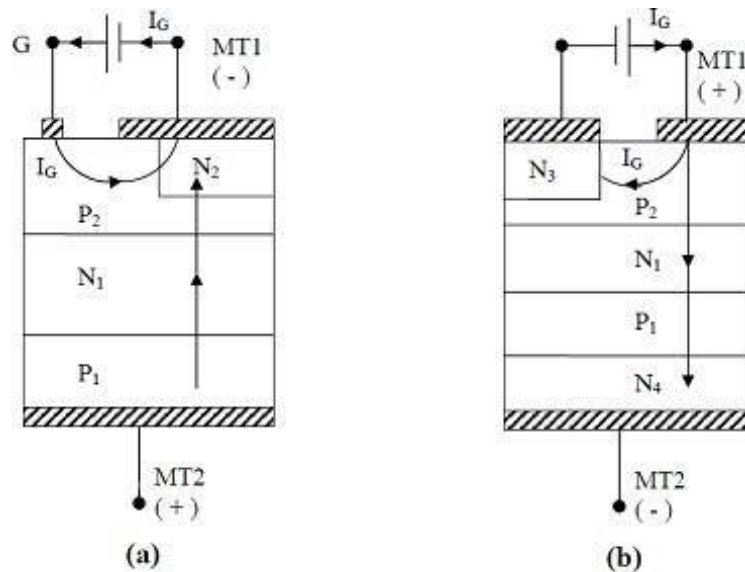

**Fig. 7** Conduction mechanism of a triac in trigger modes 1 and 3  
(a) Mode – 1 , (b) Mode – 3 .

In trigger mode-1 the gate current flows mainly through the  $P_2 N_2$  junction like an ordinary thyristor. When the gate current has injected sufficient charge into  $P_2$  layer the triac starts conducting through the  $P_1 N_1 P_2 N_2$  layers like an ordinary thyristor.

In the trigger mode-3 the gate current  $I_g$  forward biases the  $P_2 P_3$  junction and a large number of electrons are introduced in the  $P_2$  region by  $N_3$ . Finally the structure  $P_2 N_1 P_1 N_4$  turns on completely.

### Applications of TRIAC (Phase control using TRIAC)


A triac is functionally equivalent to two anti parallel connected thyristors. It can block voltages in both directions and conduct current in both directions.

- A triac has three terminals like a thyristor. It can be turned on in either half cycle by either a positive or a negative current pulse at the gate terminal.
- Triacs are extensively used at power frequency ac load (eg heater, light, motors) control applications.

## Power BJT
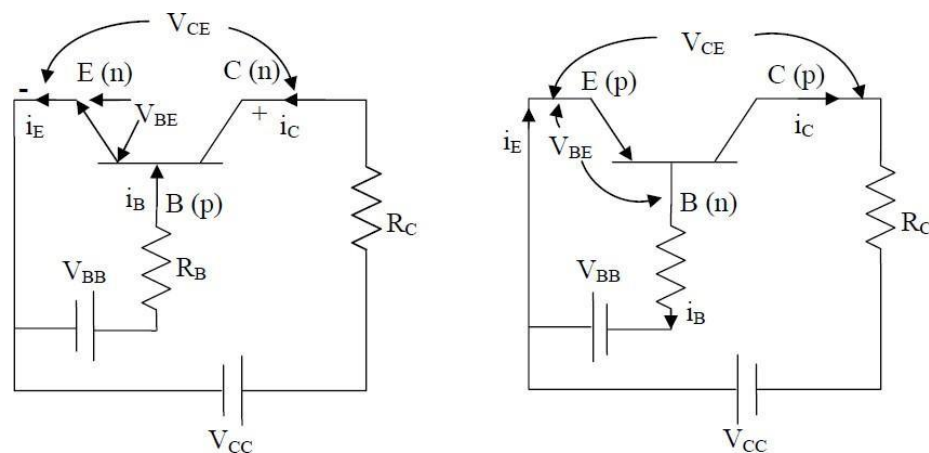
### Operation, construction of an NPN POWER Transistor as a switch

Power Bipolar Junction Transistor (BJT) is the first semiconductor device to allow full control over its Turn on and Turn off operations. It simplified the design of a large number of Power Electronic circuits that used forced commutated thyristors at that time and also helped realize a number of new circuits. BJT was the first semiconductor device to closely approximate an ideal fully controlled Power switch.



A junction transistor consists of a semiconductor crystal in which a **p** type region is sandwiched between two **n** type regions. This is called an **n-p-n** transistor. Alternatively an **n** type region may be placed in between two **p** type regions to give a **p-n-p** transistor. Fig above shows the circuit symbols and schematic representations of an **n-p-n** and a **p-n-p** transistor. The terminals of a transistor are called Emitter (E), Base (B) & Collector (C) as shown in the figure.

When a transistor is used as a controlled switch, the control current input is provided at the base terminal. The control circuit is connected between the base and emitter. The power terminals of the switch are the collector and the emitter.

The output characteristic is a plot of the current  $I_C$  through the switch versus the voltage  $V_{CE}$  across it for a fixed value of the current  $I_B$ .

Let us assume that  $V = 150 \text{ V}$ ,  $R = 30\Omega$  and decide to keep  $I_B$  at  $0.6 \text{ A}$ . The voltage  $V_{CE}$  across the switch and the current  $I_C$  through it must be given by a point on the characteristic for  $I_B = 0.6 \text{ A}$ . To locate this point, we used a second relationship by a straight line called the "load line."

$$V_{CE} = V - I_C R = 150V - I_C \cdot 30\Omega$$

What will happen if we progressively reduce the base current  $I_B$ .

$I_B$	$I_C$	$V_{CE}$	$P_{DIS}=V_{CE} I_C$
0.6 A	$\approx 5A$	$V_{CE}(SAT)\approx 2.5V$	12.5W
0.4 A	$\approx 5A$	$V_{CE}(SAT)\approx 2.5V$	12.5W
0.2 A	3A	60 V	180W

For  $I_B = 0.2$  A, the intersection point gives  $V_{CE} = 60$  V and a current of 3 A. The transistor is no longer in the saturated ON state. Such a condition is to be avoided, because, there is excessive power dissipation in the transistor (180W), which can result in its damage.

It is necessary to ensure a saturated ON state, by providing adequate base drive current, for the safe and satisfactory operation of the switch. Therefore, the minimum base current to ensure the saturated ON state is given by  $I_B = I_C / h_{FE}$  where  $h_{FE}$  is a parameter specified in the data sheet of the transistor.

Often it will be advisable to use a somewhat higher value of base current than that indicated by the above formula, as a safety feature, to take care of possible increases in  $I_C$  above the anticipated value.


### Applications of BJT in Power switching applications

There are two types of **applications of BJT**, switching and amplification.

#### Transistor as a Switch


For switching applications transistor is biased to operate in the saturation or cutoff region. Transistor in cutoff region will act as an open switching whereas in saturation will act as a closed switch.

#### Open Switch

 

In the cutoff region (both junctions are reversed biased) the voltage across the CE junction is very high. The input voltage is zero so both base and collector currents are zero, hence the resistance offered by the BJT is very high (ideally infinite).

### Closed Switch

 


In saturation (both junctions are forward biased) a high input voltage is applied to the base. The value of base resistance is adjusted such that a large base current flows. There is a small voltage drop across the collector emitter junction of the order of 0.05 to 0.2V and collector current is very large. A very small voltage drop takes place across the BJT and it can be said to be equivalent to a closed switch.



## Power MOSFET

### Operation, construction of Power MOSFET & its characteristics curve

Power MOSFET is a device that evolved from MOS integrated circuit technology. The first attempts to develop high voltage MOSFETs were by redesigning lateral MOSFET to increase their voltage blocking capacity.

 

**Fig.8** Schematic construction of a power MOSFET  
 (a) Construction of a single cell.  
 (b) Arrangement of cells in a device.


The resulting technology was called lateral double diffused MOS (DMOS). However it was soon realized that much larger breakdown voltage and current ratings could be achieved by resorting to a vertically oriented structure. Since then, vertical DMOS (VDMOS) structure


has been adapted by virtually all manufacturers of Power MOSFET. A power MOSFET using

VDMOS technology has vertically oriented three layer structure of alternating **p** type and **n** type semiconductors as shown in Fig 8 (a) which is the schematic representation of a single MOSFET cell structure. A large number of such cells are connected in parallel (as shown in Fig 8 (b)) to form a complete device

### Operation

The gate region of a MOSFET which is composed of the gate metallization, the gate (silicon) oxide layer and the p-body silicon forms a high quality capacitor. When a small voltage is application to this capacitor structure with gate terminal positive with respect to the source (note that body and source are shorted) a depletion region forms at the interface between the  $\text{SiO}_2$  and the silicon as shown in Fig 9 (a).

 

 

**Fig. 9 Gate control of MOSFET conduction.**  
 (a) Depletion layer formation;  
 (b) Free electron accumulation;  
 (c) Formation of inversion layer.

The positive charge induced on the gate metallization repels the majority hole carriers from the interface region between the gate oxide and the **p** type body. This exposes the negatively charged acceptors and a depletion region is created.

Further increase in  $V_{GS}$  causes the depletion layer to grow in thickness. At the same time the electric field at the oxide-silicon interface gets larger and begins to attract free electrons as shown in Fig 9 (b). The immediate source of electron is electron-hole generation by thermal ionization. The holes are repelled into the semiconductor bulk ahead of the depletion region. The extra holes are neutralized by electrons from the source.


As  $V_{GS}$  increases further the density of free electrons at the interface becomes equal to the free hole density in the bulk of the body region beyond the depletion layer. The layer of free electrons at the interface is called the inversion layer and is shown in Fig 9 (c). The inversion layer has all the properties of an **n** type semiconductor and is a conductive path or -channel between the drain and the source which permits flow of current between the drain and the source. Since current conduction in this device takes place through an **n**- type -channel created by the electric field due to gate source voltage it is called -Enhancement type n-channel MOSFET.

The value of  $V_{GS}$  at which the inversion layer is considered to have formed is called the -Gate - Source threshold voltage  $V_{GS(th)}$ . As  $V_{GS}$  is increased beyond  $V_{GS(th)}$  the inversion layer gets somewhat thicker and more conductive, since the density of free electrons

increases further with increase in  $V_{GS}$ . The inversion layer screens the depletion layer adjacent to it from increasing  $V_{GS}$ . The depletion layer thickness now remains constant.

### Steady state output i-v characteristics of a MOSFET

The MOSFET, like the BJT is a three terminal device where the voltage on the gate terminal controls the flow of current between the output terminals, Source and Drain. The source terminal is common between the input and the output of a MOSFET. The output characteristics of a MOSFET is then a plot of drain current ( $i_D$ ) as a function of the Drain – Source voltage ( $v_{DS}$ ) with gate source voltage ( $v_{GS}$ ) as a parameter. Fig 10 (a) shows such a characteristics.

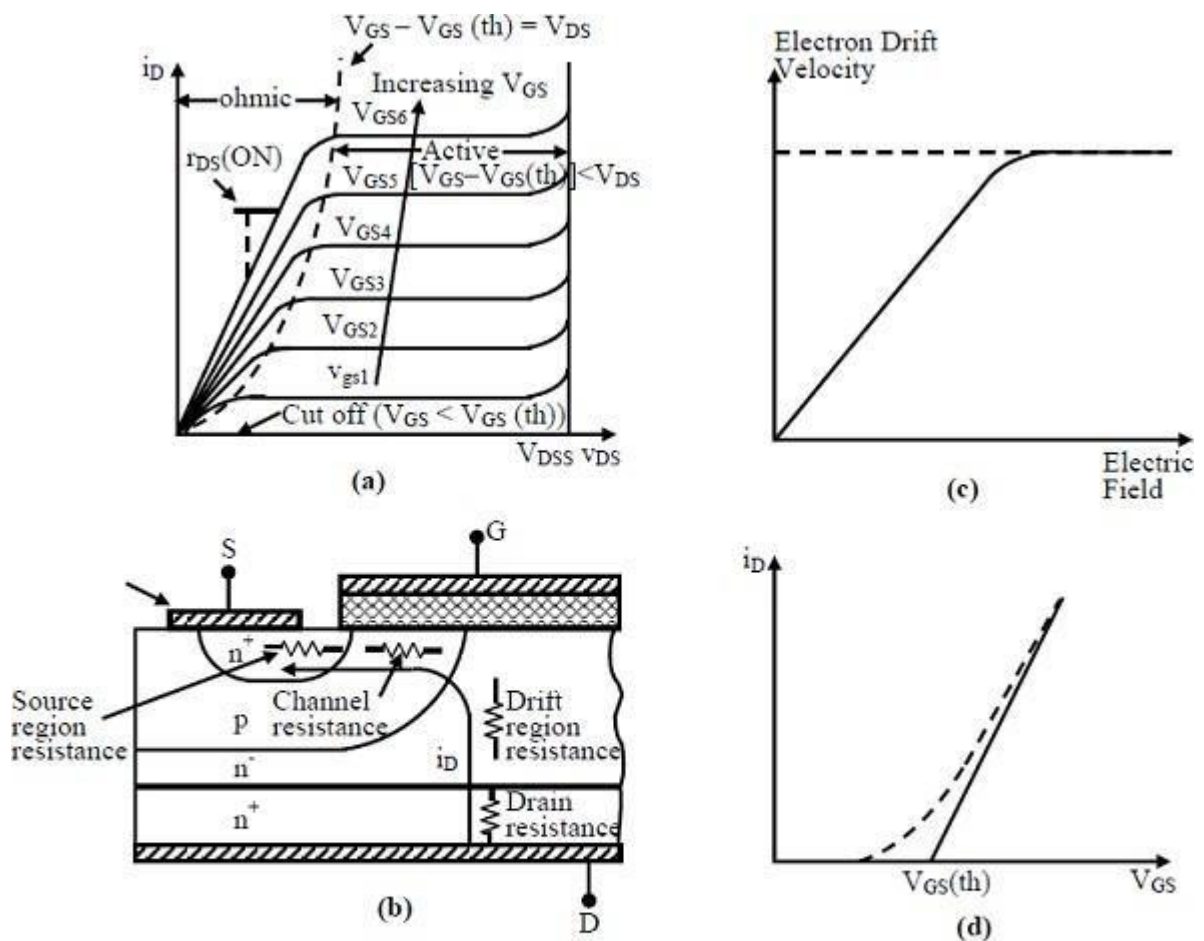

**Fig. 10 Output i-v characteristics of a Power MOSFET**

- (a) i-v characteristics;
- (b) Components of ON-state resistance;
- (c) Electron drift velocity vs Electric field;
- (d) Transfer

With gate-source voltage ( $V_{GS}$ ) below the threshold voltage ( $v_{GS(th)}$ ) the MOSFET operates in the cut-off mode. No drain current flows in this mode and the applied drain-source voltage ( $v_{DS}$ ) is supported by the body-collector **p-n** junction. Therefore, the maximum applied voltage should be below the avalanche break down voltage of this junction ( $V_{DSS}$ ) to avoid destruction of the device.

When  $V_{GS}$  is increased beyond  $v_{GS(th)}$  drain current starts flowing. For small values of  $v_{DS}$  ( $v_{DS} < (v_{GS} - v_{GS(th)})$ )  $i_D$  is almost proportional to  $v_{DS}$ . Consequently this mode of operation is called -ohmic mode of operation. In power electronic applications a MOSFET is operated either in the cut off or in the ohmic mode. The slope of the  $v_{DS} - i_D$  characteristics in this mode is called the ON state resistance of the MOSFET ( $r_{DS(ON)}$ ). Several physical resistances as shown in Fig 10 (b) contribute to  $r_{DS(ON)}$ . Note that  $r_{DS(ON)}$  reduces with increase in  $v_{GS}$ . This is mainly due to reduction of the channel resistance at higher value of

$v_{GS}$ . Hence, it is desirable in power electronic applications, to use as large a gate-source voltage as possible subject to the dielectric break down limit of the gate-oxide layer.

## **Applications of MOSFET**

### ***1 MOSFET as an analog switch***

Enhancement mode MOSFET based analog switches use the transistor channel as a low resistance to pass analog signals when on, and as a high impedance when off. Signals can flow in either direction across a MOSFET switch. In this application the drain and source of a MOSFET exchange places depending on the voltages of each electrode compared to that of the gate and the direction of current flow. For a simple MOSFET without an integrated diode from source to drain (or the back gate or body terminal tied to the source), the source is the more negative side for an NMOS or the more positive side for a PMOS. All of these switches are limited as to what signals they can pass when on or block when off by their gate-source, gate-drain and source-drain voltages, and source-to-drain currents; exceeding these voltage or current limits will potentially damage the switch.

## ***2 Switched Capacitor Circuits***


A switched capacitor is an electronic circuit element used in discrete time signal processing systems. It works by transferring charge into and out of a capacitor when switches are opened and closed. Usually, non-overlapping signals are used to control the switches, often termed Break before Make switching, so that all switches are open for a very short time during the switching transitions. Discrete time filters implemented with these elements are termed 'switched-capacitor filters'. Unlike continuous time analog filters, which must be constructed with resistors, capacitors and sometimes inductors whose values are accurately known, switched capacitor filters depend only on the ratios between capacitances and the switching frequency. This makes them much more suitable for use within integrated circuits, where the accurately specified absolute value of components such as resistors and capacitors are not economical to construct.



# GTO

## Construction, operation of GTO and V-I characteristics

### Construction

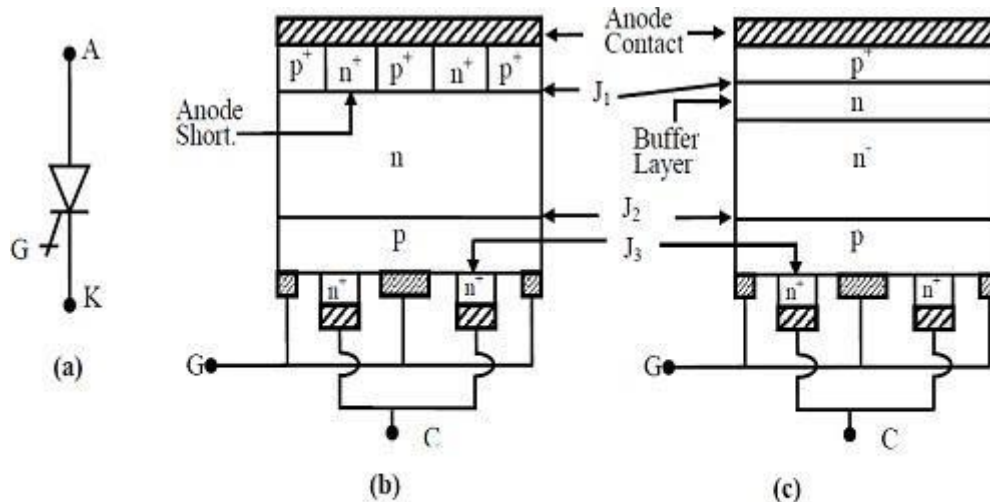

**Fig.11** Circuit symbol and schematic cross section of a GTO  
 (a) Circuit Symbol, (b) Anode shorted GTO structure,  
 (c) Buffer layer GTO structure.

Like a thyristor, a GTO is also a four layer three junction **p-n-p-n** device. In order to obtain high emitter efficiency at the cathode end, the **n** cathode layer is highly doped. Consequently, the break down voltage of the function  $J_3$  is low (typically 20-40V). The **p** type gate region has conflicting doping requirement. To maintain good emitter efficiency the doping level of this layer should be low, on the other hand, from the point of view of good turn off properties, resistivity of this layer should be as low as possible requiring the doping level of this region to be high. Therefore, the doping level of this layer is highly graded. Additionally, in order to optimize current turn off capability, the gate cathode junction must be highly interdigitated. A 3000 Amp GTO may be composed of upto 3000 individual cathode segments which are accessed via a common contact. The most popular design features multiple segments arranged in concentric rings around the device center.

The maximum forward blocking voltage of the device is determined by the doping level and the thickness of the **n** type base region next. In order to block several kv of forward voltage the doping level of this layer is kept relatively low while its thickness is made considerably higher (a few hundred microns). Beyond the maximum allowable forward voltage either the electric field at the main junction ( $J_2$ ) exceeds a critical value (avalanche break



down) or the **n** base fully depletes, allowing its electric field to touch the anode emitter (punch through).

The junction between the **n** base and **p+** anode ( $J_1$ ) is called the -anode junction. For good turn on properties the efficiency of this anode junction should be as high as possible requiring a heavily doped **p+** anode region. However, turn off capability of such a GTO will be poor with very low maximum turn off current and high losses. There are two basic approaches to solve this problem.

In the first method, heavily doped **n+** layers are introduced into the **p+** anode layer. They make contact with the same anode metallic contact. Therefore, electrons traveling through the base can directly reach the anode metal contact without causing hole injection from the **p+** anode. This is the classic -anode shorted GTO structure as shown in Fig 11 (b). Due to presence of these -anode shorts the reverse voltage blocking capacity of GTO reduces to the reverse break down

Voltage of junction  $J_3$  (20-40 volts maximum). In addition a large number of -anode shorts reduces the efficiency of the anode junction and degrades the turn on performance of the device. Therefore, the density of the -anode shorts are to be chosen by a careful compromise between the turn on and turn off performance.

### Operating principle of a GTO

GTO being a monolithic **p-n-p-n** structure just like a thyristor its basic operating principle can be explained in a manner similar to that of a thyristor. In particular, the **p-n-p-n** structure of a GTO can be thought of consisting of one **p-n-p** and one **n-p-n** transistor connected in the regenerative configuration as shown in Fig 12.

From the -two transistor analogy (Fig 12 (a)) of the GTO structure one can write.

$$i_{C1} = \alpha_p I_A + I_{CBO1} \quad (5.1)$$


$$i_{B1} = i_{C2} = \alpha_n I_k + I_{CBO2} \quad (5.2)$$

$$I_k = I_A + I_G \quad \text{and} \quad I_A = i_{B1} + i_{C1} \quad (5.3)$$

$$I_A = \frac{\alpha_n I_G + (i_{CBO1} + i_{CBO2})}{1 - (\alpha_n + \alpha_p)} \quad (5.4)$$

With applied forward voltage  $V_{AK}$  less than the forward break over voltage both  $I_{CBO1}$  and  $I_{CBO2}$  are small. Further if  $I_G$  is zero  $I_A$  is only slightly higher than  $(I_{CBO1} + I_{CBO2})$ . Under

this condition both  $a_n$  and  $a_p$  are small and  $(a_n + a_p) \ll 1$ . The device is said to be in the forward blocking mode.

 


**Fig12 Current distribution in a GTO**  
(a) During turn on; (b) During turn off.

To turn the device on either the anode voltage can be raised until  $I_{CBO1}$  and  $I_{CBO2}$  increases by avalanche multiplication process or by injecting a gate current. The current gain  $\alpha$  of silicon transistors rises rapidly as the emitter current increases. Therefore, any mechanism which causes a momentary increase in the emitter current can be used to turn on the device. Normally, this is done by injecting current into the p base region via the external gate contact. As  $a_n + a_p$  approaches unity the anode current tends to infinity. Physically as  $a_n + a_p$  nears unity the device starts to regenerate and each transistor drives its companion into saturation. Once in saturation, all junctions assume a forward bias and total potential drop across the device becomes approximately equal to that of a single **p-n** diode. The anode current is restricted only by the external circuit. Once the device has been turned on in this manner, the external gate current is no longer required to maintain conduction, since the regeneration process is self-sustaining. Reversion to the blocking mode occurs only when the anode current is brought below the -holding current level.

To turn off a conducting GTO the gate terminal is biased negative with respect to the cathode. The holes injected from the anode are, therefore, extracted from the p base through the gate metallization into the gate terminal (Fig 12 (b)). The resultant voltage drop in the p base above the n emitter starts reverse biasing the junction  $J_3$  and electron injection stops here. The process originates at the periphery of the p base and the n emitter segments and the area still injecting electron shrinks. The anode current is crowded into higher and higher density filaments in most remote areas from the gate contact. This is the most critical phase in the GTO turn off process since highly localized high temperature regions can cause device failure unless these current filaments are quickly extinguished. When the last filament disappears, electron injection stops completely and depletion layer starts to grow on both  $J_2$  and  $J_3$ . At this point the device once again starts blocking forward voltage. However, although the cathode current has ceased the anode to gate current continues to flow (Fig 12 (b)) as the n base excess carriers diffuse towards  $J_1$ . This -tail current then decays exponentially as the n base excess carriers reduce by recombination. Once the tail current has completely disappeared does the device regain its steady state blocking characteristics. -Anode Shorts (or transparent emitter) helps reduce the tail current faster by providing an alternate path to the n base electrons to reach the anode contact without causing appreciable hole injection from anode.

#### Steady state output and gate characteristics

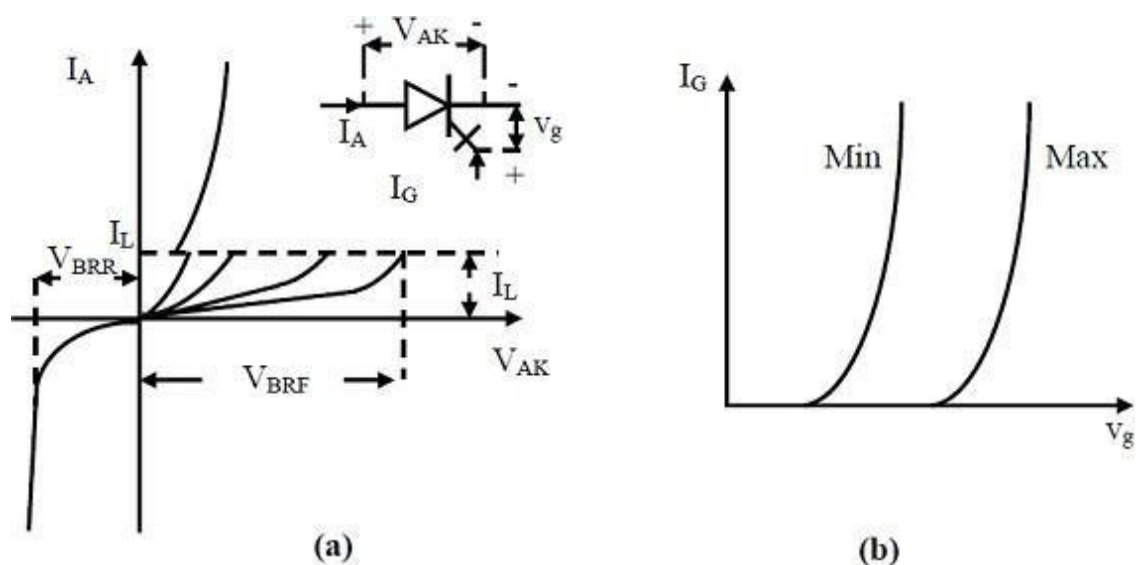

**Fig. 13 Steady state characteristics of a GTO**  
 (a) Output characteristics; (b) Gate characteristics.

This characteristic in the first quadrant is very similar to that of a thyristor as shown in Fig. 13 (a). However, the latching current of a GTO is considerably higher than a thyristor of similar rating. The forward leakage current is also considerably higher. In fact, if the gate current is not sufficient to turn on a GTO it operates as a high voltage low gain transistor with considerable anode current. It should be noted that a GTO can block rated forward voltage only when the gate is negatively biased with respect to the cathode during forward blocking state. At least, a low value resistance must be connected across the gate cathode terminal. Increasing the value of this resistance reduces the forward blocking voltage of the GTO. Asymmetric GTOs have small (20-30 V) reverse break down voltage. This may lead the device to operate in -reverse avalanche under certain conditions. This condition is not dangerous for the GTO provided the avalanche time and current are small. The gate voltage during this period must remain negative.

Fig 13 (b) shows the gate characteristics of a GTO. The zone between the min and max curves reflects parameter variation between individual GTOs. These characteristics are valid for DC and low frequency AC gate currents.

### **Application of GTO**

The main applications are in variable speed motor drives, high power inverters, static VAR compensators (SVCs) and AC/DC power supplies with high power ratings and traction. GTOs are increasingly being replaced by integrated gate-commutated thyristors, which are an evolutionary development of the GTO, and insulated gate bipolar transistors, which are members of the transistor family.

## IGBT

### Operation, construction of IGBT and its characteristics curve

#### Constructional Features of an IGBT

Vertical cross section of a n channel IGBT cell is shown in Fig 14. Although p channel IGBTs are possible n channel devices are more common


 


Fig. 14 Vertical cross section of an IGBT cell.

The major difference with the corresponding MOSFET cell structure lies in the addition of a **p+** injecting layer. This layer forms a **pn** junction with the drain layer and injects minority carriers into it. The **n** type drain layer itself may have two different doping levels. The lightly doped **n-** region is called the drain drift region. Doping level and width of this layer sets the forward blocking voltage (determined by the reverse break down voltage of  $J_2$ ) of the device. However, it does not affect the on state voltage drop of the device due to conductivity modulation as discussed in connection with the power diode. This construction of the device is called -Punch Through (PT) design. The Non-Punch Through (NPT) construction does not have this added **n+** buffer layer. The PT construction does offer lower on state voltage drop compared to the NPT construction particularly for lower voltage rated devices. However, it does so at the cost of lower reverse break down voltage for the device, since the reverse break down voltage of the junction  $J_1$  is small. The rest of the construction of the device is very similar to that of a **vertical MOSFET** including the insulated gate structure and the shorted body (**p** type) – emitter (**n+** type) structure. The doping level and physical geometry of the **p** type body region however, is considerably different from that of a MOSFET in order to defeat the latch up action of a parasitic thyristor embedded in the IGBT

structure. A large number of basic cells as shown in Fig 14 are grown on a single silicon wafer and connected in parallel to form a complete IGBT device.

 

**Fig. 15** Circuit symbol of an IGBT.  
**(a)** Circuit symbol.  
**(b)** Photograph.


### Operating principle of an IGBT

Operating principle of an IGBT can be explained in terms of the schematic cellstructure and equivalent circuit of Fig 16(a) and (c). From the input side the IGBT behaves essentially as a MOSFET. Therefore, when the gate emitter voltage is less than the threshold voltage no inversion layer is formed in the **p** type body region and the device is in the off state. The forward voltage applied between the collector and the emitter drops almost entirely across the junction  $J_2$ . Very small leakage current flows through the device under this condition. In terms of the equivalent circuit of Fig 16(c), when the gate emitter voltage is lower than the threshold voltage the driving MOSFET of the Darlington configuration remains off and hence the output **p-n-p** transistor also remains off.

When the gate emitter voltage exceeds the threshold, an inversion layer forms in the **p** type body region under the gate. This inversion layer (channel) shorts the emitter and the drain drift layer and an electron current flows from the emitter through this channel to the drain drift region. This in turn causes substantial hole injection from the **p+** type collector to the drain drift region. A portion of these holes recombine with the electrons arriving at the drain drift region through the channel. The rest of the holes cross the drift region to reach the **p** type body where they are collected by the source metallization.

From the above discussion it is clear that the **n** type drain drift region acts as the base of the output **p-n-p** transistor. The doping level and the thickness of this layer determines the current gain  $\beta$  of the **p-n-p** transistor. This is intentionally kept low so that most of the device current flows through the MOSFET and not the output **p-n-p** transistor collector. This

helps to reduced the voltage drop across the -body// spreading resistance shown in Fig 16 (b) and eliminate the possibility of static latch up of the IGBT.

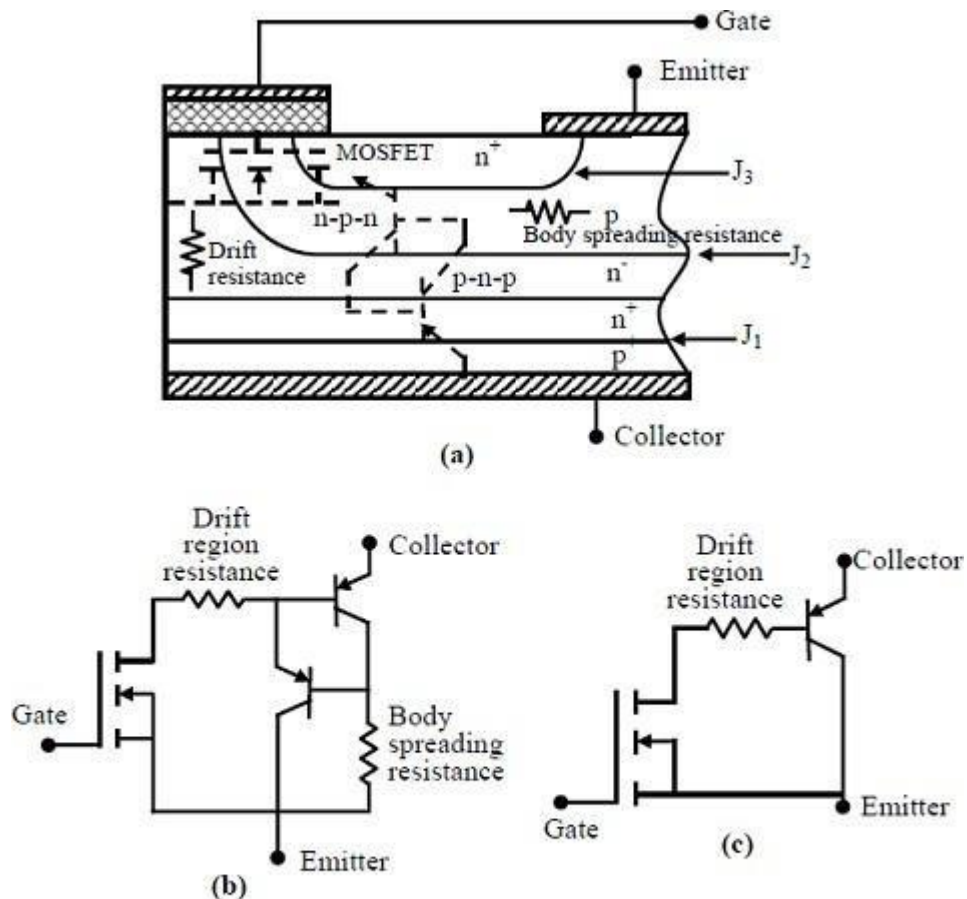


**Fig.16** Parasitic thyristor in an IGBT cell.  
 (a) Schematic structure  
 (b) Exact equivalent circuit.  
 (c) Approximate equivalent circuit

The total on state voltage drop across a conducting IGBT has three components. The voltage drop across  $J_1$  follows the usual exponential law of a **pn** junction. The next component of the voltage drop is due to the drain drift region resistance. This component in an IGBT is considerably lower compared to a MOSFET due to strong conductivity modulation by the injected minority carriers from the collector. This is the main reason for reduced voltage drop across an IGBT compared to an equivalent MOSFET. The last component of the voltage drop across an IGBT is due to the channel resistance and its magnitude is equal to that of a comparable MOSFET.



### Steady state characteristics of an IGBT

The  $i$ - $v$  characteristics of an n channel IGBT is shown in Fig 17 (a). They appear qualitatively similar to those of a logic level BJT except that the controlling parameter is not a base current but the gate-emitter voltage.

 

**Fig. 17 Static characteristics of an IGBT**  
(a) Output characteristics; (b) Transfer characteristics

When the gate emitter voltage is below the threshold voltage only a very small leakage current flows through the device while the collector – emitter voltage almost equals the supply voltage (point C in Fig 17(a)). The device, under this condition is said to be operating in the cut off region. The maximum forward voltage the device can withstand in this mode (marked  $V_{CES}$  in Fig 17 (a)) is determined by the avalanche break down voltage of the body – drain **p-n** junction. Unlike a BJT, however, this break down voltage is independent of the collector current as shown in Fig 17(a). IGBTs of Non-punch through design can block a maximum reverse voltage ( $V_{RM}$ ) equal to  $V_{CES}$  in the cut off mode. However, for Punch Through IGBTs  $V_{RM}$  is negligible due to the presence of the heavily doped **n+** drain buffer layer.

As the gate emitter voltage increases beyond the threshold voltage the IGBT enters into the active region of operation. In this mode, the collector current  $i_c$  is determined by the transfer characteristics of the device as shown in Fig 17(b). This characteristic is qualitatively similar to that of a power MOSFET and is reasonably linear over most of the collector current range. The ratio of  $i_c$  to  $(V_{GE} - v_{GE(th)})$  is called the forward transconductance ( $g_{fs}$ ) of the device and is an important parameter in the gate drive circuit design. The collector emitter voltage, on the other hand, is determined by the external load line ABC as shown in Fig 17(a).



As the gate emitter voltage is increased further  $i_c$  also increases and for a given load resistance ( $R_L$ )  $v_{CE}$  decreases. At one point  $v_{CE}$  becomes less than  $v_{gE} - v_{gE(th)}$ . Under this

condition the driving MOSFET part of the IGBT (Fig 16(c)) enters into the ohmic region and drives the output **p-n-p** transistor to saturation. Under this condition the device is said to be in the saturation mode. In the saturation mode the voltage drop across the IGBT remains almost constant reducing only slightly with increasing  $v_{gE}$ .

In power electronic applications an IGBT is operated either in the cut off or in the saturation region of the output characteristics. Since  $v_{CE}$  decreases with increasing  $v_{gE}$ , it is desirable to use the maximum permissible value of  $v_{gE}$  in the ON state of the device.  $v_{gE(Max)}$  is limited by the maximum collector current that should be permitted to flow in the IGBT as dictated by the -latch-up condition discussed earlier. Limiting  $V_{gE}$  also helps to limit the fault current through the device. If a short circuit fault occurs in the load resistance  $R_L$  (shown in the inset of Fig 17(a)) the fault load line is given by CF. Limiting  $v_{gE}$  to  $v_{gE6}$  restricts the fault current corresponding to the operating point F. Most IGBTs are designed to withstand this fault current for a few microseconds within which the device must be turned off to prevent destruction of the device.

**Applications of IGBT:** IGBTs are used in high power applications such as:

- Appliance motor drives
- Electric vehicle motor drives
- Power factor correction converters
- Uninterruptible power supplies
- Solar inverters
- High frequency welders
- Inductive heating cookers

## Chapter – 2 SCR CONTROL CIRCUITS

SCR or silicon controlled rectifier is a controlled device and it behaves as a short circuit while in the on state and as open circuit when in off condition.

### Turn On Methods

#### Describe briefly different methods of TURN ON of an SCR

Turn-on method is otherwise known as triggering method. The turning on Process of the SCR is known as Triggering. In other words, turning the SCR from Forward-Blocking state to Forward-Conduction state is known as Triggering.

The various SCR triggering methods are

- Forward Voltage Triggering
- Thermal or Temperature Triggering
- Radiation or Light triggering
- $dv/dt$  Triggering
- Gate Triggering

#### (a) **Forward Voltage Triggering:-**

In this mode, an additional forward voltage is applied between anode and cathode. When the anode terminal is positive with respect to cathode ( $V_{AK}$ ), Junction  $J_1$  and  $J_3$  is forward biased and junction  $J_2$  is reverse biased. No current flows due to depletion region in  $J_2$  is reverse biased (except leakage current). As  $V_{AK}$  is further increased, at a voltage  $V_{BO}$  (Forward Break Over Voltage) the junction  $J_2$  undergoes avalanche breakdown and so a current flows and the device tends to turn ON (even when gate is open)

#### (b) **Thermal (or) Temperature Triggering:-**

The width of depletion layer of SCR decreases with increase in junction temperature. Therefore in SCR when  $V_{AR}$  is very near its breakdown voltage, the device is triggered by increasing the junction temperature. By increasing the junction temperature the reverse biased junction collapses thus the device starts to conduct.

#### (c) **Radiation Triggering (or) Light Triggering:-**

For light triggered SCRs a special terminal niche is made inside the inner P layer instead of gate terminal. When light is allowed to strike this terminal, free charge carriers are generated. When intensity of light becomes more than a normal value, the thyristor starts conducting. This type of SCRs are called as LASCR

**(d) dv/dt Triggering:-**

When the device is forward biased,  $J_1$  and  $J_3$  are forward biased,  $J_2$  is reverse biased. Junction  $J_2$  behaves as a capacitor, due to the charges existing across the junction. If voltage across the device is  $V$ , the charge by  $Q$  and capacitance by  $C$  then,

$$i_c = dQ/dt$$

$$Q = CV$$

$$i_c = d(CV)/dt = C.dV/dt + V.dC/dt$$

$$\text{As } dC/dt = 0, i_c = C.dV/dt$$

Therefore when the rate of change of voltage across the device becomes large, the device may turn ON, even if the voltage across the device is small.

**(e) Gate Triggering:-**

This is most widely used SCR triggering method. Applying a positive voltage between gate and cathode can Turn ON a forward biased thyristor. When a positive voltage is applied at the gate terminal, charge carriers are injected in the inner P-layer, thereby reducing the depletion layer thickness. As the applied voltage increases, the carrier injection increases, therefore the voltage at which forward break-over occurs decreases.

**General functions to be fulfilled by gate control circuits**

The gate control circuit is also called the firing circuit and a firing circuit should fulfill the following two functions.

(i) If power circuit has more than one SCR, the firing circuit should produce gating pulses for each SCR at the desired instant for proper operation of the power circuit.

These pulses must be periodic in nature and the sequence of firing must correspond with the type of thyristorised power controller.

(ii) Before giving the voltage pulses to the firing circuit, the voltage pulses should be fed to a driver circuit. The reason is that the control signal generated by a firing circuit may not be able to turn-on the SCR.


**Firing Circuits****General layout diagram of firing circuit**

The different firing circuits used are

- R-firing circuit
- RC-firing circuit
- UJT pulse trigger circuit

- T Synchronous triggering (Ramp Triggering ) circuit
 
### R firing circuits or Resistance triggering circuit:




The following circuit shows the resistance triggering. In this method, the variable resistance  $R$  is used to control the gate current.

Depending upon the value of  $R$ , when the magnitude of the gate current reaches the sufficient value (latching current of the device) the SCR starts to conduct. The diode  $D$  is called as blocking diode. It prevents the gate cathode junction from getting damaged in the negative half cycle. By considering that the gate circuit is purely resistive, the gate current is in phase with the applied voltage. By using this method we can achieve maximum firing angle up to  $90^\circ$ .
 
### RC-firing circuit

The following circuit shows the resistance-capacitance triggering.



By using this method we can achieve firing angle more than  $90^\circ$ . In the positive half cycle, the capacitor is charged through the variable resistance  $R$  up to the peak value of the applied voltage. The variable resistor  $R$  controls the charging time of the capacitor. Depends upon the voltage across the capacitor, when sufficient amount of gate current will flow in the circuit, the SCR starts to conduct. In the negative half cycle, the capacitor  $C$  is charged up to the negative peak value through the diode  $D2$ . Diode  $D1$  is used to prevent the reverse break down of the gate cathode junction in the negative half cycle.

## UJT pulse trigger circuit

One common application of the Uni-junction transistor is the triggering of the other devices such as the SCR, triac etc. The basic elements of such a triggering circuit are shown in figure. The resistor  $R_E$  is chosen so that the load line determined by  $R_E$  passes through the device characteristic in the negative resistance region, that is, to the right of the peak point but to the left of the valley point, as shown in figure. If the load line does not pass to the right of the peak point P, the device cannot turn on.

For ensuring turn-on of UJT  $R_E < V_{BB} - V_P / I_P$

This can be established as below

Consider the peak point at which  $I_{RE} = I_P$  and  $V_E = V_P$

(the equality  $I_{RE} = I_P$  is valid because the charging current of capacitor, at this instant is zero, that is, the capacitor, at this particular instant, is changing from a charging state to a discharging state).

Then  $V_E = V_{BB} - I_{RE} R_E$

So,  $R_{E(MAX)} = V_{BB} - V_E / I_{RE} = V_{BB} - V_P / I_P$  at the peak point.

At the valley point, V

$I_E = I_V$  and  $V_E = V_V$  so that

$V_E = V_{BB} - I_{RE} R_E$

So  $R_{E(MIN)} = V_{BB} - V_E / I_{RE} = V_{BB} - V_V / I_V$  or for ensuring turn-off.


$R_E > V_{BB} - V_V / I_V$

So, the range of resistor  $R_E$  is given as

$V_{BB} - V_P / I_P > R_E > V_{BB} - V_V / I_V$

The resistor R is chosen small enough so as to ensure that SCR is not turned on by voltage  $V_R$  when emitter terminal E is open or  $I_E = 0$

 
The voltage  $V_R = R V_{BB} / R + R_{BB}$  for open-emitter terminal.




The capacitor  $C$  determines the time interval between triggering pulses and the time duration of each pulse. By varying  $R_E$ , we can change the time constant  $R_E C$  and alter the point at which the UJT fires. This allows us to control the conduction angle of the SCR, which means the control of load current.
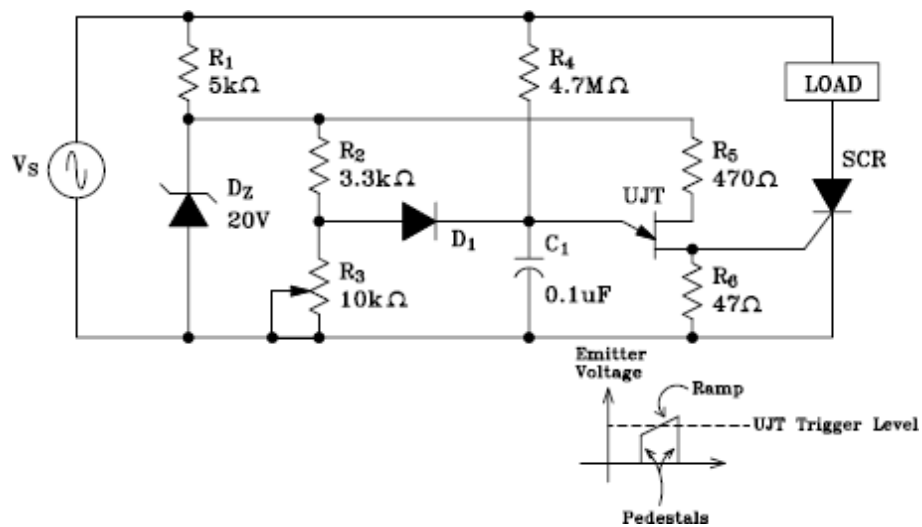
### Ramp-Pedestal UJT-SCR Control Circuit:

The circuit, shown below, uses a UJT to trigger a SCR. The UJT is used to more accurately trigger the SCR. When the source voltage exceeds 20V, the zener diode ( $D_Z$ ) will begin to conduct, applying a DC voltage across the base connections of the UJT. At the same time, diode  $D_1$  will be forward biased, and the capacitor will quickly charge through  $R_1$  and  $R_2$ . This represents the left-hand pedestal portion of the emitter voltage.



 Once the capacitor charges to the voltage across  $R_3$ ,  $D_1$  will become reverse biased and the capacitor will continue to slowly charge through  $R_4$ . This represents the ramp portion of the emitter voltage.



The capacitor continues to charge until the UJT fires. At this point the capacitor will quickly discharge through  $R_6$ , and this represents the right-hand pedestal of the emitter voltage. The capacitor discharge is sufficient to trigger the SCR. The point at which the UJT fires can be adjusted by varying the pot  $R_3$ . With a large setting on  $R_3$ , the capacitor must charge to a larger value before  $D_2$  becomes reverse biased. This causes the UJT to fire faster, resulting in more of the source voltage appearing across the SCR. This can be seen graphically as shown in the fig.

## **Turn-off methods (Communication Schemes)**

The term commutation basically means the transfer of current from one path to another. It is not possible for a thyristor to turn itself OFF; the circuit in which it is connected must reduce the thyristor current to zero to enable it to turn-off.

### **Definition**

‘COMMUTATION’ is the term to describe the methods of achieving this, or it is defined as the process of turning-off a thyristor.

### **List different types of communication methods**

Broadly classified into two methods:

1. Natural commutation
2. Forced commutation

#### **Natural commutation**

This widely used method of commutation makes use of the alternating, reversing nature of a.c voltage to effect the current transfer. As the current passes through natural zero, a reverse voltage will simultaneously appear across the device. This immediately turns-off the device. This process is called as natural commutation since no external circuit is required for this purpose.

#### **Forced commutation**

In case of d.c circuits, for switching off the thyristors, the forward current should be forced to be zero by means of some external circuits. The process is called forced commutation.

#### **Classification of forced commutation techniques**

The classification is based on the arrangement of commutating components and the manner in which zero current is obtained in the SCR. The six distinct classes by which the SCR can be turned off are:

Class A Self commutated by a resonating load



Class B Self commutated by a L-C circuit

Class C C or L-C switched by another load carrying SCR otherwise known as Complementary commutation

Class D C or L-C switched by an auxiliary SCR, known as Auxiliary commutation


Class E An external pulse source for commutation, also known as External pulse commutation

Class F or AC line commutation or natural commutation

### **Different commutation with circuit diagram and waveforms**
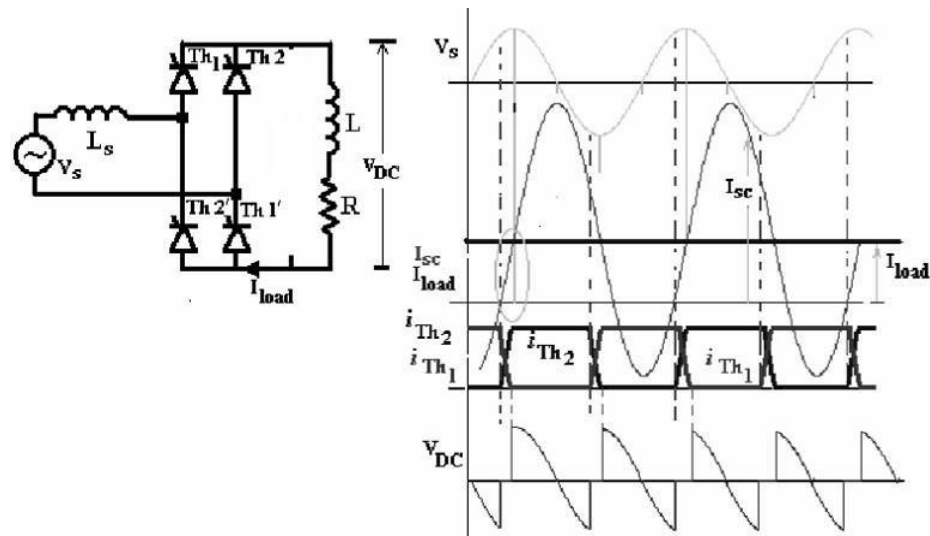
#### **a) Line commutation or Class-F commutation**


If the supply is an alternating voltage, load current will flow during the positive half cycle. With a highly inductive load, the current may remain continuous for some time till the energy trapped in the load inductance is dissipated. During the negative half cycle, therefore, the SCR will turn off when the load current becomes zero 'naturally'. The negative polarity of the voltage appearing across the outgoing SCR turns it off if the voltage persists for the rated turnoff period of the device. The duration of the half cycle must be definitely longer than the turnoff time of the SCR. The rectifier in the below figure is supplied from a single phase AC supply. The commutation process involved here is representative of that in a three phase converter. The converter has an input inductance  $L_s$  arising mainly out of the leakage reactance of the supply transformer. Initially, SCRs  $Th_1$  and  $Th_1'$  are considered to be conducting. The triggering angle for the converter is around  $60^\circ$ . The converter is operating in the continuous conduction mode aided by the highly-inductive load. When the incoming SCRs,  $Th_2$  and  $Th_2'$  are triggered, the current through the incoming devices cannot rise instantaneously to the load current level. A circulating current  $I_{sc}$  builds up in the short-circuited path including the supply voltage,  $V_s$ - $L_s$ - $Th_1$ - $Th_2$  and  $V_s$ - $L_s$ - $Th_2'$ - $Th_1'$  paths. The period when both the devices conduct is known as the 'overlap period'. Since all SCRs are in conduction, the output voltage for this period is zero. If the 'fully-controlled' converter in the figure is used as an inverter with triggering angles  $> 90^\circ$ , the converter triggering can be delayed till the 'margin angle' which includes the overlap angle and the turn-off time of the SCR - both dependent on the supply voltages.



Class F, natural commutation by supply voltage
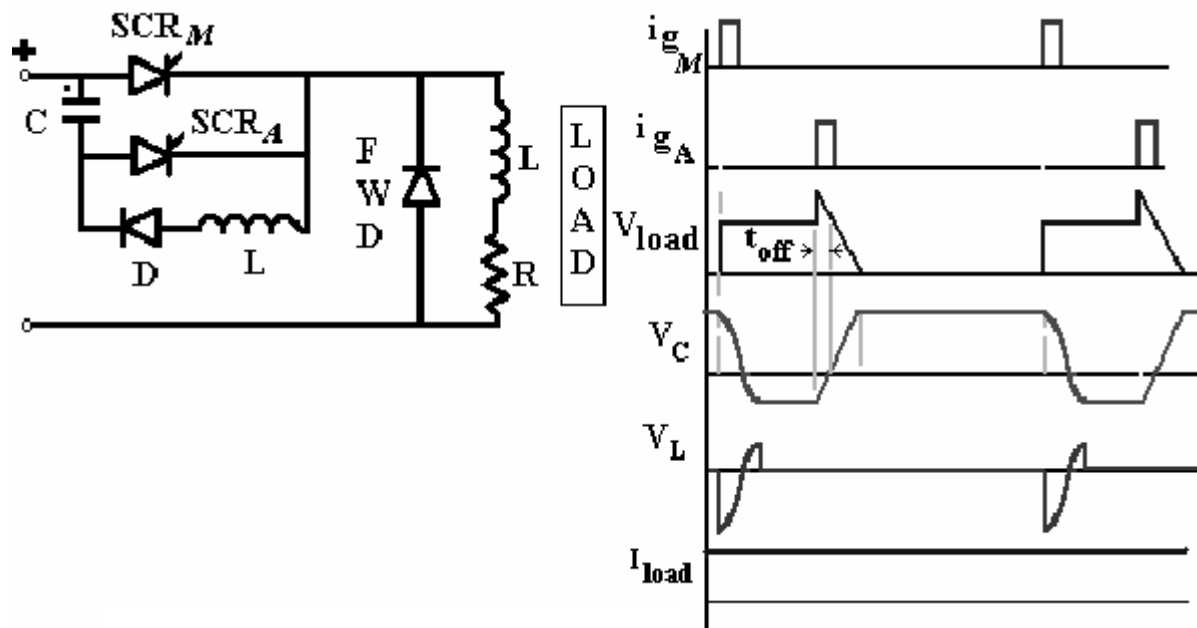
### b) Auxiliary voltage commutation or Class-D commutation

The following circuit is used for auxiliary voltage commutation.  $SCR_A$  must be triggered first in order to charge the upper terminal of the capacitor as positive. As soon as  $C$  is charged to the supply voltage,  $SCR_A$  will turn off.




When  $SCR_M$  is triggered the current flows in two paths:

- Load current flows through the load and
- The commutating current flows through  $C$ -  $SCR_M$  - $L$ - $D$  network.

The charge on  $C$  is reversed and held at that level by the diode  $D$ . When  $SCR_A$  is re-triggered, the voltage across  $C$  appears across  $SCR_M$  via  $SCR_A$  and  $SCR_M$  is turned off. If the load carries a constant current as in Fig. the capacitor again charges linearly to the dot as positive.

 **c) Resonant commutation or Class-A commutation**



When the SCR is triggered, anode current flows and charges up  $C$  with the dot as positive. The L-C-R forms a second order under-damped circuit. The current through the SCR builds up and completes a half cycle. When the inductor current will then attempt to flow through the SCR in the reverse direction and the SCR will be turned off. Load can be either in parallel with capacitance or in series with the capacitance as in fig below. The capacitor voltage is at its peak when the SCR turns off and the capacitor discharges into the resistance in an exponential manner. The SCR is reverse-biased till the capacitor voltage returns to the level of the supply voltage  $V$ .

## Chapter-3 CONTROLLED RECTIFIER

### Introduction


Single phase fully controlled bridge converters are widely used in many industrial applications. They can supply unidirectional current with both positive and negative voltage polarity. Thus they can operate either as a controlled rectifier or an inverter. The inverter mode of operation of a single phase fully controlled converter is made possible by the forward voltage blocking capability of the thyristors which allows the output voltage to go negative. The disadvantages of the single phase fully controlled converter are also related to the same capability.

### Application

Used in high voltage DC transmission, electrometallurgical process, magnetic power supplies, electroplating, battery charging, speed control of Dc drives, Traction.

**Controlled rectifiers Techniques (Phase Angle, Extinction Angle control & PWM) and 3.3 principle of phase control and definition of firing angle (alpha) and Conduction angle (beta) with schematic diagram and waveforms for half wave controlled rectifier**

### Principle of phase control

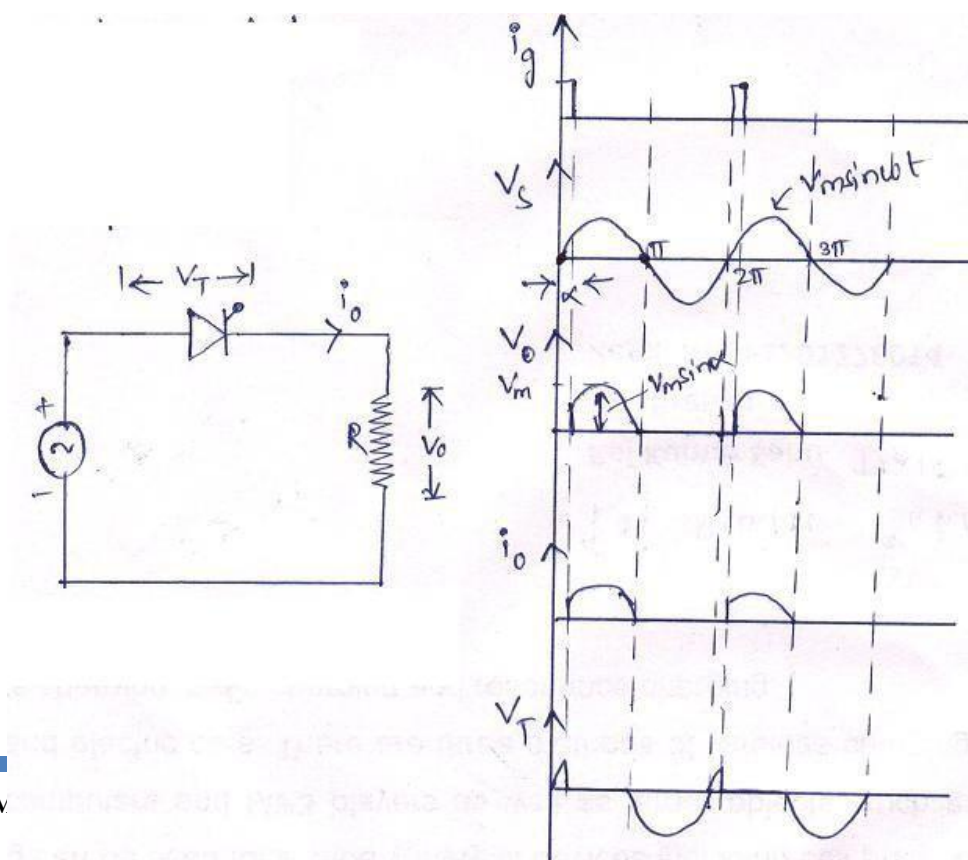

A simple controlled rectifier circuit consists of a single thyristor feeding dc power to a resistive load  $R$ . source voltage is  $v_s = v_m \sin \omega t$ .

An SCR can conduct only when anode voltage is positive and a gating signal is applied. A thyristor blocks the flow of load current  $i_o$  until it is triggered.

At some delay angle  $\alpha$ , a positive gate signal is applied between gate and cathode turns on the SCR. Immediately full supply voltage is applied to the load as  $v_o$ .

**Firing Angle( $\alpha$ ):** - It is the angle between the instant at which the thyristor would conduct, if it was a diode, and the instant at which it is triggered.

It can also be defined as the angle measured from the instant SCR gets forward biased to the instant it is triggered.

**Conduction Angle( $\gamma$ ):** - it is defined as the angle during the period in which the SCR is in conduction state.

**Extinction Angle( $\beta$ ):** - it is the angle measured from the reference point to the instant at which the current extinguishes to zero.

Relation between  $\beta$ ,  $\gamma$  and  $\alpha$

$$\beta = \alpha + \gamma$$

### **Classification of converters: -**

The phase controlled converters may be classified as semi-converter, full converter, dual converter. Depending on the input ac supply used they are classified as single phase and three phase converters.

**Semi-converter:** -A semi-converter is a one quadrant converter and it has one polarity of output voltage and current. It contains a mixture of diodes and thyristors allowing more limited control over the dc output voltage level than the full controlled rectifier. It is cheaper. It permits power flow from AC system to DC load. It is also known as half-wave controlled converter.

**Full-converter:** -A full-converter is a two-quadrant converter and the polarity of its output voltage can be either positive or negative. However, the output current of full-converter has one polarity only. Here power can be transmitted from AC side to DC side (conversion) and from DC side to AC side (inversion). It uses only thyristor as rectifying elements.

**Dual-converter:** -If two full converters are connected back to back they form a dual converter. It can operate in four quadrants and both the output voltage and current can be either positive or negative. Normally these are used in high power applications.

### 3.4 Integral Cycle Control (ICC)

For power transfer two types of controls are normally used. One is on-off control or integral cycle control and another is phase angle control.


In integral-cycle control, thyristor switches connect the load to the ac source for a few cycles of input voltage and disconnects it for another few cycles.

The ICC is otherwise known as burst firing or zero voltage switching or cycle selection.
 
#### Single phase fully controlled bridge converter with Resistive load only (with & without FD)

The figure shows the circuit diagram of a single phase fully controlled bridge converter. It is one of the most popular converter circuits and is widely used in the speed control of separately excited dc machines.

The single phase fully controlled bridge converter is obtained by replacing all the diode of the corresponding uncontrolled converter by thyristors. Thyristors  $T_1$  and  $T_2$  are fired together while  $T_3$  and  $T_4$  are fired  $180^\circ$  after  $T_1$  and  $T_2$ . From the circuit diagram of Fig 10.3(a) it is clear that for any load current to flow at least one thyristor from the top group ( $T_1, T_3$ ) and one thyristor from the bottom group ( $T_2, T_4$ ) must conduct and neither  $T_1T_3$  nor  $T_2T_4$  can conduct simultaneously. Whenever  $T_3$  and  $T_4$  are in the forward blocking state and a gate pulse is applied to them, they turn ON and at the same time a negative voltage is applied across  $T_1$  and  $T_2$  commutating them immediately. Similar is the case for  $T_1$  and  $T_2$ .



The only possible conduction modes when the current  $i_0$  can flow are T1T2 and T3T4. It may happen that at a given moment none of the thyristors conduct. This situation will typically occur when the load current becomes zero in between the firings of T1T2 and T3T4. Once the load current becomes zero all thyristors remain off.

In this mode the load current remains zero. Consequently the converter is said to be operating in the discontinuous conduction mode. Figure shows the voltage across different devices and the dc output voltage during each of these conduction modes. It is to be noted that whenever T1 and T2 conducts, the voltage across T3 and T4 becomes  $-v_i$ . Therefore T3 and T4 can be fired only when  $v_i$  is negative i.e, over the negative half cycle of the input supply voltage. Similarly T1 and T2 can be fired only over the positive half cycle of the input supply. The voltage across the devices when none of the thyristors conduct depends on the off state impedance of each device.

Under normal operating condition of the converter the load current may or may not remain zero over some interval of the input voltage cycle. If  $i_0$  is always greater than zero then the converter is said to be operating in the continuous conduction mode. In this mode of operation of the converter T1T2 and T3T4 conducts for alternate half cycle of the input supply.

**Explain with circuit diagram and waveforms the operation of fully controlled three phase bridge converter with Resistive load (with & without FD)**

### **3Φ full Converter using Bridge Circuit**

3Φ phase power supply are connected in two ways.

- (1) Star connection
- (2) Delta connection

In a 3Φ full converter bridge rectifier circuit two thyristor phases are required each phase with 6 SCR in a circuit. This configuration utilizes both the positive and negative portion of input signal.

The thyristors are fired at an interval of  $\pi/3$  at  $wt = (\pi/6) + \alpha$ .

The thyristor are fired at an interval of  $\pi/3$  at  $wt = \pi/6 + \alpha$ , thyristor T6 is already conducting & thyristor T1 is turned on. During the interval  $(\pi/6 + \alpha) \leq wt \leq (\pi/2 + \alpha)$  thyristor T1 & T6 are conduct the line to line voltage  $V_{ab} = V_{an} - V_{bn}$  appears across the load. At  $wt = (\pi/2) + \alpha$  thyristor T2 is fired & thyristor T6 reverse biased immediately T6 is turned off due to natural commutation. During the interval  $(\pi/2 + \alpha) \leq wt \leq (5\pi/6 + \alpha)$  thyristor T1 & T2 conduct & the line to line voltage  $V_{ac}$  appears across the load. The firing sequence is 12,23,34,45,56,61



## LINE TO NEUTRAL VOLTAGE

Let

$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = V_m \sin (\omega t - 2\pi/3)$$

$$V_{cn} = V_m \sin (\omega t + 2\pi/3)$$

Line to line voltage is

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin (\omega t + \pi/6)$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_m \sin (\omega t - \pi/2)$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_m \sin (\omega t + \pi/2)$$

The average o/p voltage

$$V_{dc} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{6} + \alpha + \frac{\pi}{6}} V_{ab} d(\omega t)$$

$$= \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{6} + \alpha + \frac{\pi}{6}} \sqrt{3} V_m \sin (\omega t + \frac{\pi}{6}) d(\omega t)$$


$$= \frac{3\sqrt{3}}{\pi} V_m \cos \alpha \quad \text{For } \alpha=0$$

$$V_{dm} = \frac{3\sqrt{3} V_m}{\pi}$$
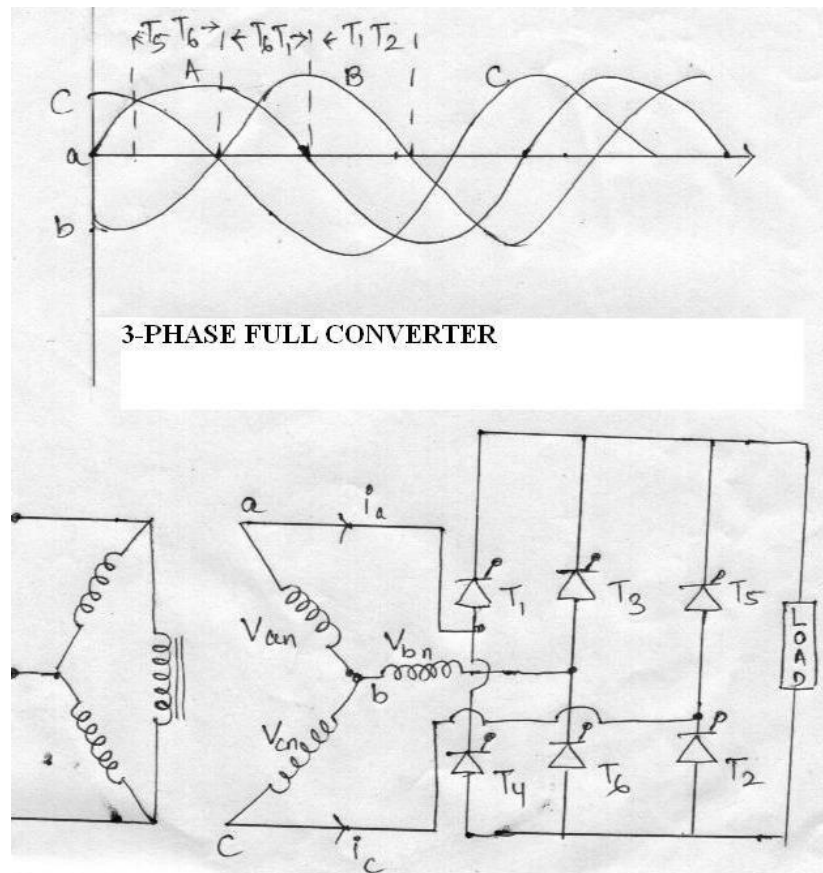
### GATING SEQUENCE:-

Generate a pulse signal at the +ve zero crossing of the phase voltage  $V_m$  delay the pulse the desired angle  $\alpha + \pi/6$  & apply it to the gate & cathode terminal of T1 through a gate isolating ckt.

Generate 5 more pulses each delayed by  $\pi/6$  from each other for getting T1, T2, T3, T4, T5 & T6 respectively through gate isolating ckt.





## Chapter-4 CHOPPER

### Define chopper & its applications.

The fixed voltage of a dc source can be converted to a variable average voltage on a load by placing a high speed switch between the dc source and the load. This high speed static switch is called chopper. This high speed switch used may be a thyristor or a BJT or an IGBT or a power MOSFET or may be a GTO depending on the application.

Thus a chopper is a power electronic device that converts a power directly from fixed dc to variable dc. In other words a chopper is a dc to dc converter.

There are three basic types of dc-dc converter circuits, termed as buck, boost and buck-boost. In all of these circuits, a power device is used as a switch. The buck converter (dc-dc) is called as 'step-down chopper', whereas boost converter (dc-dc) is a 'step-up chopper'.

#### Applications of chopper

Choppers find their applications in traction motors, trolley cars, hoists and also in variable speed ac and dc drives.

The advantages of chopper include smooth speed control, low losses, high efficiency, fast dynamic response and regeneration capability when applied in drive control.

### Principle of operation of

#### • Step down chopper (Buck converts)

A buck converter (dc-dc) is shown in the below figure. Only a switch is shown in this figure. Also a diode (termed as freewheeling) is used to allow the load current to flow through it, when the switch (i.e., a device) is turned off.

 


Fig. 17.1(a): Buck converter (dc-dc)

The load is inductive (R-L) one. Due to the load inductance, the load current must be allowed a path, which is provided by the diode; otherwise, i.e., in the absence of the above

diode, the high induced emf of the inductance, as the load current tends to decrease, may cause damage to the switching device. If the switching device used is a thyristor, this circuit is called as a step-down chopper, as the output voltage is normally lower than the input voltage. The output voltage and current waveforms of the circuit are shown below.

 


Fig. 17.1(b): Output voltage and current waveforms

The output voltage is same as the input voltage, i.e.,  $V_s = V_o$ , when the switch is ON, during the period,  $T_{ON} \geq t \geq 0$ . The switch is turned on at  $t = 0$ , and then turned off at  $t = T_{ON}$ . This is called ON period.

During the next time interval,  $T \geq t \geq T_{ON}$ , the output voltage is zero, i.e.,  $V_o = 0$ , as the diode  $D_F$ , now conducts.

The OFF period is  $T_{OFF} = T - T_{ON}$  with the time period being

$$T = T_{ON} + T_{OFF}.$$


The frequency is  $f = 1/T$ .

The duty ratio is  $k = T_{ON}/T = (T_{ON})/(T_{ON} + T_{OFF})$ ,

its range being  $1.0 \geq k \geq 0.0$

## • Step down chopper (Boost converts)


A boost converter (dc-dc) is shown in below figure. A diode is used in series with the load. An inductance,  $L$  is assumed in series with the input supply. First the switch,  $S$  (i.e., the device) is put ON (or turned ON) during the period,  $T_{ON} \geq t \geq 0$  the ON period being  $T_{ON}$ . The output voltage is zero if no battery (back emf) is connected in series with the load, The current from the source ( $i_s$ ) flows in the inductance  $L$ . The value of current increases linearly with time in this interval, with  $(di/dt)$  being positive.

 

**Fig. 17.2(a): Boost converter (dc-dc)**

As the current through  $L$  increases, the polarity of the induced emf is taken as say, positive, the left hand side of  $L$  being +ve. The equation for the circuit is,

$$V_s = L \frac{di_s}{dt} \quad \text{or,} \quad \frac{di_s}{dt} = \frac{V_s}{L}$$

 

**Fig. 17.2(b): Waveforms of source current ( $i_s$ )**


The switch,  $S$  is put OFF during the period,  $T \geq t \geq T_{ON}$ .

As the current through  $L$  decreases, with its direction being in the same direction as shown (same as in the earlier case), the induced emf reverses, the left hand side of  $L$  being -ve. So, the induced emf (taken as -ve in the equation given later) is added with the supply voltage, being of the same polarity, thus, keeping the current  $i_s = i_0$  in the same direction. The current  $i_s = i_0$  decreases linearly in the time interval,  $T_{OFF}$  as the output voltage is assumed to be nearly constant. In this case, the output voltage is higher than the input voltage, as

contrasted with the previous case of buck converter (dc-dc). So, this is called boost converter (dc-dc), when a self-commutated device is used as a switch.

- **Step up & Down chopper (Buck Boost converts)**

The below figure shows a buck-boost converter. The connection of the diode may be noted, as compared with its connection in a boost Converter. The inductor,  $L$  is connected in parallel after the switch and before the diode. The load is of the same type as given earlier. A capacitor,  $C$  is connected in parallel with the load. The polarity of the output voltage is opposite to that of input voltage here. When the switch,  $S$  is put ON, the supply current(is) flows through the path,  $V_s$ -S-L during the time interval,  $T_{ON}$  The currents through both source and inductor increase and are same, with  $di_L/dt$  being positive.

 


**Fig. 17.3(a): Buck-boost converter (dc-dc)**

The polarity of the induced voltage is same as that of the input voltage. The equation for the circuit is,

$$V_s = L \frac{di_L}{dt} \quad \text{or,} \quad \frac{di_L}{dt} = \frac{V_s}{L}$$

Then, the switch,  $S$  is put OFF. The inductor current tends to decrease, with the polarity of the induced emf reversing.  $di_L/dt$  is negative now, the polarity of the output voltage,  $V_0$  being opposite to that of the input voltage,  $V_s$ .

 

**Fig. 17.3(b): Inductor current ( $i_L$ ) waveform**

The path of the current is through L, parallel combination of load & C, and diode D, during the time interval,  $T_{OFF}$ . The output voltage remains nearly constant, as the capacitor is connected across the load.

### **Control Strategies of chopper (TRC & Current unit)**

In all cases, it is shown that the average value of the output voltage can be varied. The two types of control strategies (schemes) are employed in all cases. These are:

- (a) Time-ratio control, and (b) Current limit control

#### **Time-ratio control (TRC)**

In the time ratio control the value of the duty ratio,  $k = T_{ON}/T$  is varied. There are two ways, which are constant frequency operation, and variable frequency operation.

#### **Constant Frequency Operation**

In this control strategy, the ON time,  $T_{ON}$  is varied, keeping the frequency or time period  $f = 1/T$  constant. This is also called as pulse width modulation control (PWM).

Two cases with duty ratios,  $k$  as (a) 0.25 (25%), and (b) 0.75 (75%) are shown in the below figure. Hence, the output voltage can be varied by varying ON time,  $T_{ON}$ .

 


Fig. 17.4: Pulse-width modulation control (constant frequency)

### Variable Frequency Operation

In this control strategy, the frequency ( $f = 1/T$ ), or time period  $T$  is varied, keeping either (a) the ON time,  $T_{ON}$  constant, or (b) the OFF time,  $T_{OFF}$  constant.

 


Fig. 17.5: Output voltage waveforms for variable frequency system

This is also called as frequency modulation control. Two cases with (a) the ON time, constant, and (b) the OFF time, constant, with variable frequency or time period are shown in below figure. The output voltage can be varied in both cases, with the change in duty ratio,  $k = T_{ON}/T$ .

## Different chopper configuration

(Single quadrant class A and class B, Two quadrant class C and class D & Four quadrant class E)


### Classification Of Choppers

Depending on their operation Choppers are classified as follows.

1. Class A Chopper
2. Class B Chopper
3. Class C Chopper
4. Class D Chopper
5. Class E Chopper

 
### Single quadrant class A

When chopper is ON, supply voltage  $V$  is connected across the load. When chopper is OFF,  $v_o = 0$  and the load current continues to flow in the same direction through the FWD (Freewheeling diode). The average values of output voltage and current are always positive. Class A Chopper is a step-down chopper in which power always flows from source to load.




*Class A Chopper is a first quadrant chopper.*

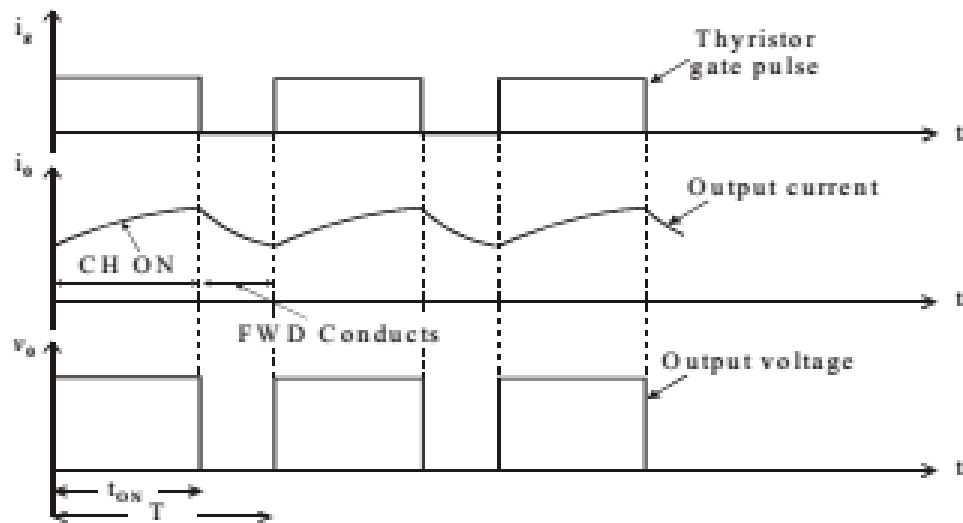It is used to control the speed of dc motor. The output current equations obtained in step down chopper with R-L load can be used to study the performance of Class A Chopper. It is used to control the speed of dc motor. The output current equations obtained in step down chopper with R-L load can be used to study the performance of Class A Chopper.


 
### Second Quadrant Class B Chopper


When chopper is ON, E drives a current through L and R in a direction opposite to that shown in figure.



*Class B Chopper operates in second quadrant*


During the ON period of the chopper, the inductance L stores energy. When Chopper is OFF, diode D conducts, and part of the energy stored in inductor L is returned to the supply. Average output voltage is positive and average output current is negative. In this chopper, power flows from load to source. Class B Chopper is used for regenerative braking of dc motor. Class B Chopper is a step-up chopper.



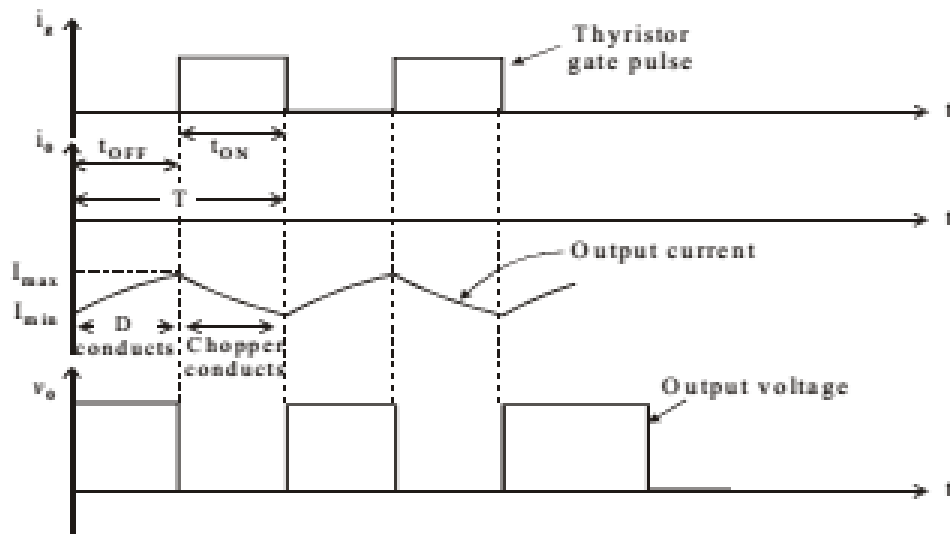
 
### Two Quadrant Class-C Chopper

Class C Chopper is a combination of Class A and Class B Choppers. For first quadrant operation,  $CH_1$  is ON or  $D_2$  conducts.




For second quadrant operation,  $CH_2$  is ON or  $D_1$  conducts. When  $CH_1$  is ON, the load current is positive. The output voltage is equal to  $V$  & the load receives power from the source. When  $CH_1$  is turned OFF, energy stored in inductance  $L$  forces current to flow through the diode  $D_2$  and the output voltage is zero. Current continues to flow in positive direction.

When  $CH_2$  is triggered, the voltage  $E$  forces current to flow in opposite direction through  $L$  and  $CH_2$ . The output voltage is zero. On turning OFF  $CH_2$ , the energy stored in the inductance drives current through diode  $D_1$  and the supply. Output voltage is  $V$ , the input current becomes negative and power flows from load to source. Average output voltage is positive. Average output current can take both positive and negative values. Choppers  $CH_1$  &  $CH_2$  should not be


turned ON simultaneously as it would result in short circuiting the supply.

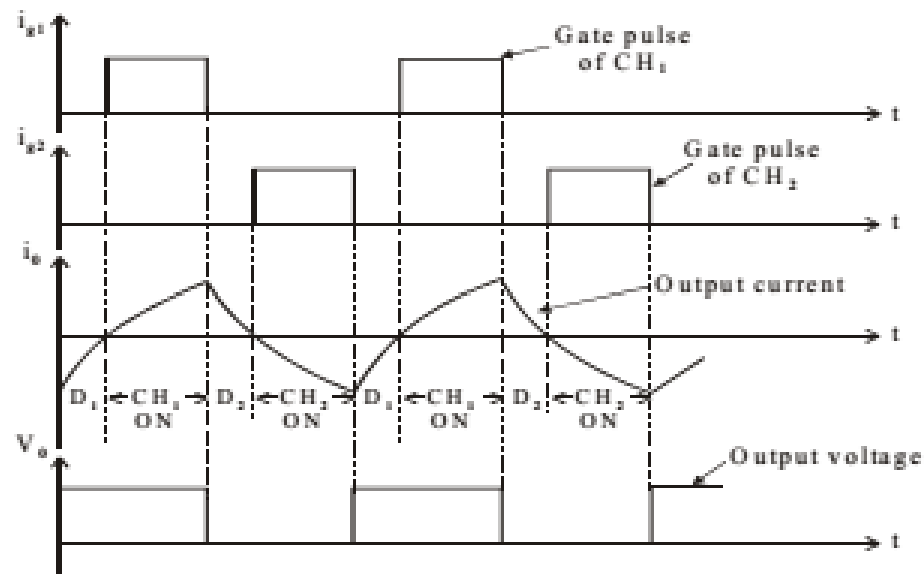Class C Chopper can be used both for dc motor control and regenerative braking of dc motor.  
Class C Chopper can be used as a step-up or step-down chopper.




### Two Quadrant Class-D Chopper


Class D is a two quadrant chopper.

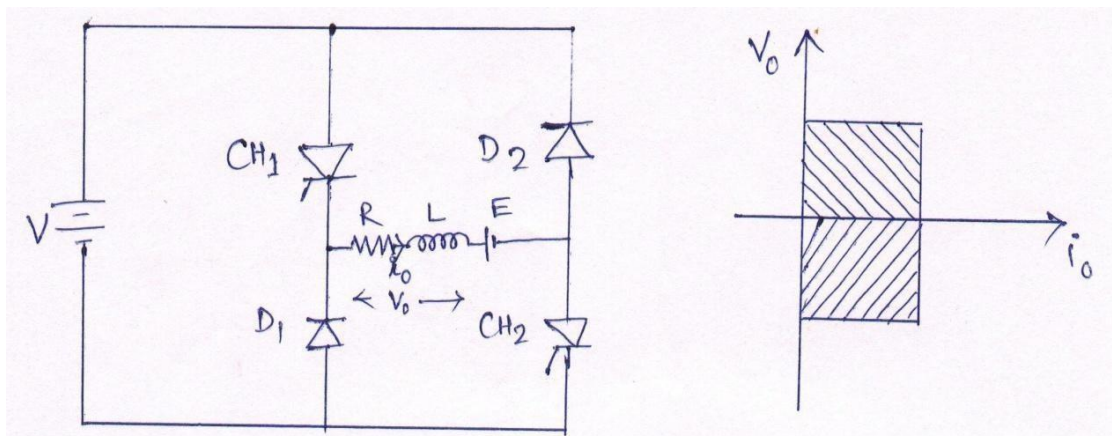

When both  $CH_1$  and  $CH_2$  are triggered simultaneously, the output voltage  $v_o = V$  and output current flows through the load. When  $CH_1$  and  $CH_2$  are turned OFF, the load current continues to flow in the same direction through load,  $D_1$  and  $D_2$ , due to the energy stored in the inductor  $L$ . Output voltage  $v_o = -V$ . Average load voltage is positive if chopper ON time is more than the OFF time. Average output voltage becomes negative if  $t_{ON} < t_{OFF}$ . Hence the direction of load current is always positive but load voltage can be positive or negative.

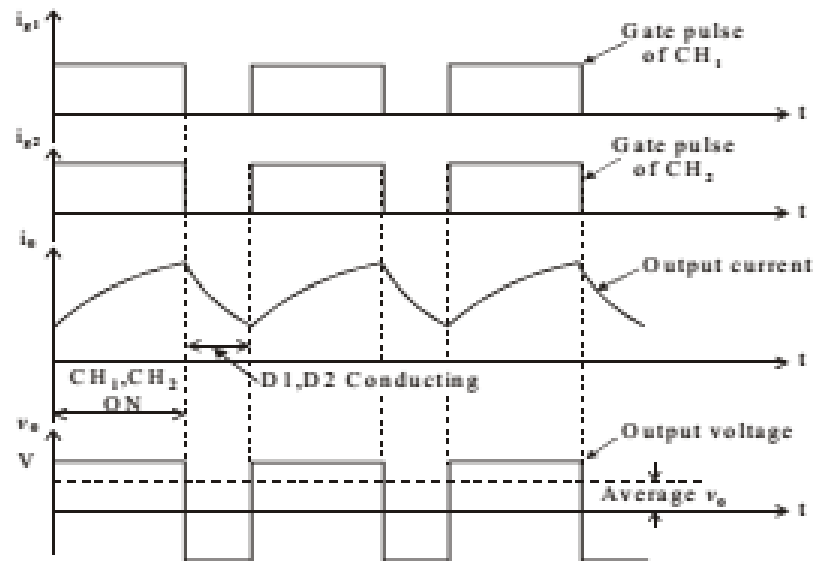


### Four Quadrant Class-E Chopper

 

Class E is a four quadrant chopper. When  $CH_1$  and  $CH_4$  are triggered, output current  $i_o$  flows in positive direction through  $CH_1$  and  $CH_4$ , and with output voltage  $v_o = V$ . This gives the first quadrant operation. When both  $CH_1$  and  $CH_4$  are OFF, the energy stored in the inductor  $L$  drives  $i_o$  through  $D_2$  and  $D_3$  in the same direction, but output voltage  $v_o$ . Therefore the chopper operates in the fourth quadrant. When  $CH_2$  and  $CH_3$  are triggered, the load current  $i_o$  flows in opposite direction & output voltage  $v_o = -V$ . Since both  $i_o$  and  $v_o$  are negative, the chopper operates in third quadrant. When both  $CH_2$  and  $CH_3$  are OFF, the load current  $i_o$  continues to flow in the same direction  $D_1$  and  $D_4$  and the output voltage  $v_o = V$ . Therefore the chopper operates in second quadrant as  $v_o$  is positive but  $i_o$  is negative.

## Four Quadrant Operation

 

## Chapter-5. Inverters

The word ‘inverter’ in the context of power-electronics denotes a class of power conversion (or power conditioning) circuits that operates from a dc voltage source or a dc current source and converts it into ac voltage or current. The ‘inverter’ does reverse of what ‘ac-to-dc converter’ does (refer to *ac to dc converters*).

Inverter is a device which converts dc power to ac power at a desired output voltage and frequency (or at a desired current level and frequency).

### Classification of inverters

Inverters can be broadly classified into two types, viz. voltage source inverter (VSI) and current source inverter (CSI).

According to the connection of semiconductor devices they are classified as (1) Bridge inverter (2) Series inverter and (3) Parallel inverter.

The nomenclature ‘inverter’ is sometimes also used for ac to dc converter circuits if the power flow direction is from dc to ac side.

‘Inverter’ is referred as a circuit that operates from a stiff dc source and generates ac output. If the input dc is a voltage source, the inverter is called a voltage source inverter (VSI). Similarly a current source inverter (CSI) is one, where the input to the circuit is a current source.


The VSI circuit has direct control over ‘output (ac) voltage’ whereas the CSI directly controls ‘output (ac) current’. Shape of voltage waveforms output by an ideal VSI should be independent of load connected.

### Single phase half bridge voltage source inverter

A single-phase square wave type voltage source inverter produces square shaped output voltage for a single-phase load. Such inverters have very simple control logic and the power switches need to operate at much lower frequencies compared to switches in some other types of inverters.

It is assumed that the input dc voltage ( $E_{dc}$ ) is constant and the switches are lossless. In half bridge topology the input dc voltage is split in two equal parts through an ideal and lossless capacitive potential divider. The half bridge topology consists of one leg (one pole) of switches whereas the full bridge topology has two such legs. Each leg of the inverter consists

 of two series connected electronic switches shown within dotted lines in the figures. Each of these switches consists of an IGBT type controlled switch across which an uncontrolled diode is put in anti-parallel manner.




**A 1-phase half bridge VSI**

These switches are capable of conducting bi-directional current but they need to block only one polarity of voltage. In half bridge topology the single-phase load is connected between the mid-point of the input dc supply and the junction point of the two switches (in Fig. above these points are marked as  $O$  and  $A$  respectively). For ease of understanding, the switches Sw1 and Sw2 may be assumed to be controlled mechanical switches that open and close in response to the switch control signal. Now, if the switches Sw1 and Sw2 are turned on alternately with duty ratio of each switch kept equal to 0.5, the load voltage ( $V_{AO}$ ) will be square wave with a peak-to-peak magnitude equal to input dc voltage ( $E_{dc}$ ). Fig. shows a typical load voltage waveform output by the half bridge inverter.  $V_{AO}$  acquires a magnitude of  $+0.5 E_{dc}$  when Sw1 is on and the magnitude reverses to  $-0.5 E_{dc}$  when Sw2 is turned on. The peak-to-peak magnitude of the fundamental frequency component of the square wave voltage, is equal to  $4/\pi E_{dc}$ . The two switches of the inverter leg are turned on in a complementary manner. For

a general load, the switches should neither be simultaneously on



 
nor be simultaneously off. Simultaneous turn-on of both the switches will amount to short circuit across the dc bus and will cause the switch currents to rise rapidly.



Square wave load voltage output by half-bridge inverter
 
## Single-Phase Full Bridge Inverter

The single-phase full bridge circuit (Fig. shown below) can be thought of as two half bridge circuits sharing the same dc bus.



A 1-phase full-bridge VSI

The full bridge circuit will have two pole-voltages ( $V_{AO}$  and  $V_{BO}$ ), which are similar to the pole voltage  $V_{AO}$  of the half bridge circuit. Both  $V_{AO}$  and  $V_{BO}$  of the full bridge circuit are square waves but they will, in general, have some phase difference. Fig. shows these pole

voltages staggered in time by  $\underline{t'}$  seconds. It may be more convenient to talk in terms of the phase displacement angle  $\underline{\Phi'}$  defined as below:

$$\Phi = (2\pi) t'/T \text{ Radians. .... (i) ,}$$


where  $\underline{t'}$  is the time by which the two pole voltages are staggered and  $\underline{T'}$  is the time period of the square wave pole voltages.

The pole voltage  $V_{AO}$  of the full bridge inverter may again be written as in Eqn.(i), used earlier for the half bridge inverter. Taking the phase shift angle  $\underline{\Phi'}$  into account, the pole-B voltage may be written as

$$V_{BO} = \sum_{n=1,3,5,7,\dots,\infty} \frac{2E_{dc}}{n\pi} \sin n(\omega t - \Phi)$$

Difference of  $V_{AO}$  and  $V_{BO}$  gives the line voltage  $V_{AB}$ . In full bridge inverter the single phase load is connected between points  $\underline{A'}$  and  $\underline{B'}$  and the voltage of interest is the load voltage  $V_{AB}$ . Taking difference of the voltage expressions we get
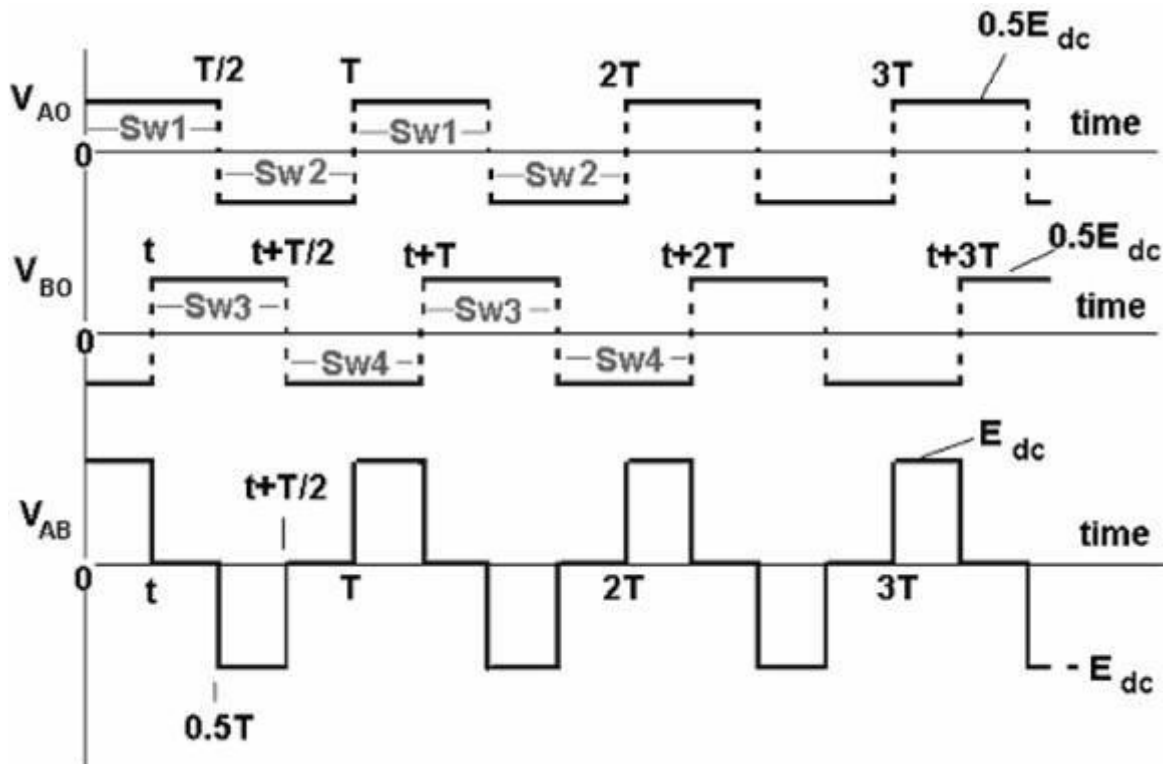
$$V_{AB} = \sum_{n=1,3,5,7,\dots,\infty} \frac{2E_{dc}}{n\pi} [\sin n\omega t - \sin n(\omega t - \Phi)]$$




Pole and line voltages output by 1-ph. full bridge inverter
 
## Three phase bridge inverter


A 3-phase bridge type VSI with square wave pole voltages is described below. The output from this inverter is to be fed to a 3-phase balanced load. The below figure shows the power circuit of the three-phase inverter. This circuit may be identified as three single-phase half-bridge inverter circuits put across the same dc bus. The individual pole voltages of the 3-phase bridge circuit are identical to the square pole voltages output by single phase half bridge or full bridge circuits. The three pole voltages of the 3-phase square wave inverter are shifted in time by one third of the output time period.

It may be seen that with the chosen numbering the switches turn on in the sequence:- Sw1, Sw2, Sw3, Sw4, Sw5, Sw6, Sw1, Sw2,....and so on. Identifying the switching cycle time as 360 degrees ( $2\pi$  radians), it can be seen that each switch conducts for  $180^\circ$  and the turning on of the adjacent switch is staggered by 60 degrees. The upper and lower switches of each pole (leg) of the inverter conduct in a complementary manner. To reverse the output phase sequence, the switching sequence may simply be reversed.



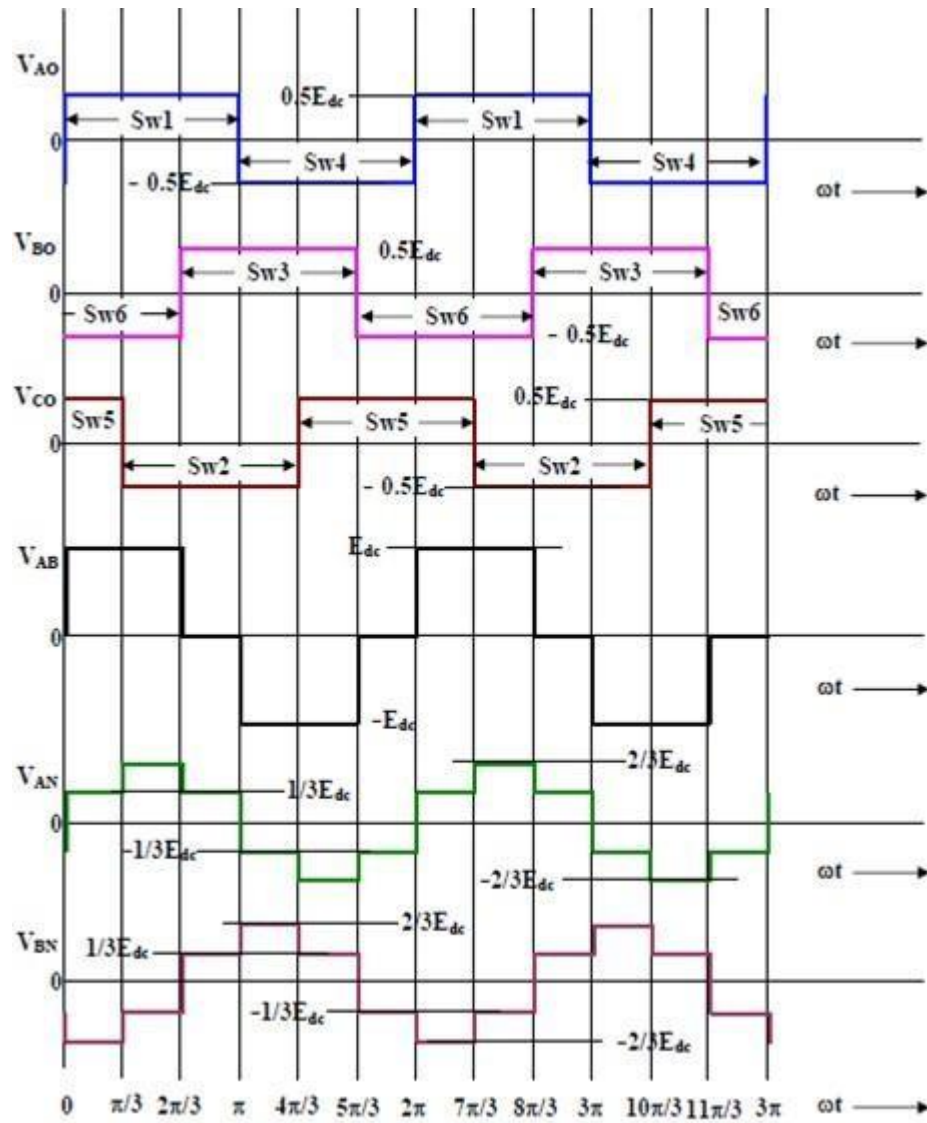**A 3-phase Voltage Source Inverter (VSI) feeding a balanced load**

Considering the symmetry in the switch conduction pattern, it may be found that at any time three switches conduct. It could be two from the upper group of switches, which are connected to positive dc bus, and one from lower group or vice-versa (i.e., one from upper group and two from lower group). According to the conduction pattern indicated in waveform diagram there are six combinations of conducting switches during an output cycle: - (Sw5, Sw6, Sw1), (Sw6, Sw1, Sw2), (Sw1, Sw2, Sw3), (Sw2, Sw3, Sw4), (Sw3, Sw4, Sw5), (Sw4, Sw5, Sw6). Each of these combinations of switches conducts for  $60^\circ$  in the sequence mentioned above to produce output phase sequence of A, B, C.



Some relevant voltage waveforms output by a 3-phase square wave VSI

## Applications of inverter

Inverters are used in variable speed ac motor drives, induction heating, UPS (uninterruptible power supplies), stand-by air-craft power supplies, HVDC transmission line, regulated voltage and frequency power supply.

## Chapter-6. CYCLOCONVERTER

The cyclo-converter is a type of power controller, where an alternating voltage at supply frequency is converted directly to an alternating voltage at load frequency (normally lower), without any intermediate dc stage.

Simply, it can be defined as a device that converts ac power at one frequency to ac power at a different frequency with single stage conversion.

### Types of Cycloconverter

Depending on frequency cycloconverters are of two types, viz. Step-up cycloconverter and Step-down cycloconverter.

In step-up type cycloconverter the output frequency ( $f_0$ ) is greater than the supply or input frequency ( $f_s$ ) i.e.  $f_0 > f_s$

In step-down type the output frequency is less than the input frequency, i.e.  $f_0 < f_s$ . Similarly depending on supply it is of 3 types, viz. 1- $\Phi$  to 1- $\Phi$ , 3- $\Phi$  to 3- $\Phi$  and 3- $\Phi$  to 1- $\Phi$ . Also depending on the type of connection it is of mid-point type or bridge type.

### Applications of cycloconverter

Its various applications include speed control of high power ac drives, induction heating, static VAR compensation. Also used for converting variable speed alternator voltage to constant frequency output voltage for use as power supply in aircraft or chip-boards.

### Advantages and Disadvantages of Cyclo-converter

#### Advantages

1. In a cycloconverter, ac power at one frequency is converted directly to a lower frequency in a single conversion stage.
2. Cycloconverter functions by means of phase commutation, without auxiliary forced commutation circuits. The power circuit is more compact, eliminating circuit losses associated with forced commutation.
3. Cycloconverter is inherently capable of power transfer in either direction between source and load. It can supply power to loads at any power factor, and is also capable of regeneration over the complete speed range, down to standstill. This feature makes it preferable for large reversing drives requiring rapid acceleration and deceleration, thus suited for metal rolling application.
4. Commutation failure causes a short circuit of ac supply. But, if an individual fuse blows off, a complete shutdown is not necessary, and cycloconverter continues to function with somewhat distorted waveforms. A balanced load is presented to the ac supply with unbalanced output conditions.

5. Cycloconverter delivers a high quality sinusoidal waveform at low output frequencies, since it is fabricated from a large number of segments of the supply waveform. This is often preferable for very low speed applications.

6. Cycloconverter is extremely attractive for large power, low speed drives.

#### **Disadvantages**

1. Large number of thyristors is required in a cycloconverter, and its control circuitry becomes more complex. It is not justified to use it for small installations, but is economical for units above 20 kVA.

2. For reasonable power output and efficiency, the output frequency is limited to one-third of the input frequency.

3. The power factor is low particularly at reduced output voltages, as phase control is used with high firing delay angle.



### **Operation of Single-phase to Single-phase Cyclo-converter**

The circuit of a single-phase to single-phase cyclo-converter is shown in the below figure. Two full-wave fully controlled bridge converter circuits, using four thyristors for each bridge, are connected in opposite direction (back to back), with both bridges being fed from ac supply (50 Hz). Bridge 1 (P – positive) supplies load current in the positive half of the output cycle, while bridge 2 (N – negative) supplies load current in the negative half. The two bridges should not conduct together as this will produce short-circuit at the input. In this case, two thyristors come in series with each voltage source.
 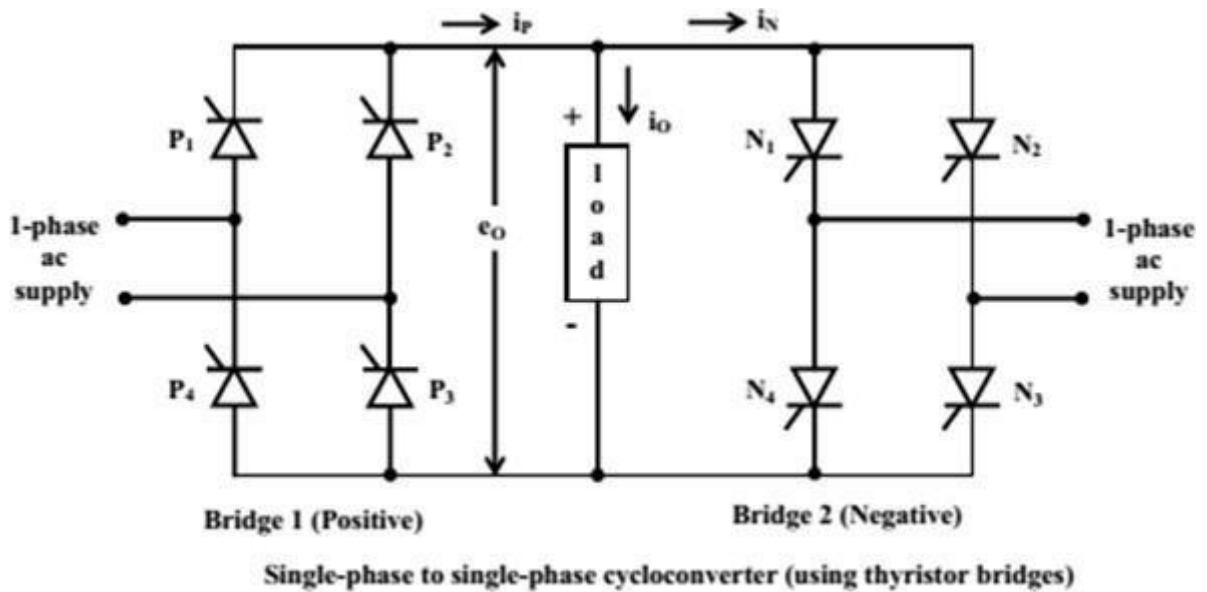
#### **Resistive (R) Load:**

For this load, the load current (instantaneous) goes to zero, as the input voltage at the end of each half cycle (both positive and negative) reaches zero (0).

Thus, the conducting thyristor pair in one of the bridges turns off at that time, i.e. the thyristors undergo natural commutation. So, operation with discontinuous current takes place (as shown in the waveform), as current flows in the load, only when the next thyristor pair in that bridge is triggered, or pulses are fed at respective gates. Taking first bridge 1 (positive), and assuming the top point of the ac supply as positive with the bottom point as negative in the positive half cycle of ac input, the odd numbered thyristor pair,  $P_1$  &  $P_3$  is triggered after phase delay ( $\alpha_1$ ), such that current starts flowing through the load in this half cycle. In the next (negative) half cycle, the other thyristor pair (even-numbered),  $P_2$  &  $P_4$  in that bridge conducts, by triggering them after suitable phase delay from the start of zero-crossing. The current flows through the load in the same direction, with the output voltage also remaining positive. This process continues for one more half cycle (making a total of three) of input voltage ( $=f_1$  50 Hz).



To obtain negative output voltage, in the next three half cycles of input voltage, bridge 2 is used. Following same logic, if the bottom point of the ac supply is taken as positive with the top point as negative in the negative half of ac input, the odd-numbered thyristor pair,  $N_1$  &  $N_3$  conducts, by triggering them after suitable phase delay from the zero-crossing. Similarly, the even-numbered thyristor pair,  $N_2$  &  $N_4$  conducts in the next half cycle.

Both the output voltage and current are now negative. As in the previous case, the above process also continues for three consecutive half cycles of input voltage.



## Chapter-7 Protection, Ratings & failure of Power Electronics Devices

### Give specification, ratings and nomenclature of Thyristors

The performance of an SCR is affected by the junction temperature, because of change in carrier densities in the four layers and the junction temperature naturally depends upon the internal power losses of the device and the efficiency of heat transfer mechanism. The factors contributing toward rise in junction temperature are

- On-state voltage drop across the device (SCR),
- Leakage current in the blocking or off state and
- Power dissipation at gate.

There are three types of ratings for an SCR like continuous; repetitive and non-repetitive. Because the SCR has a short thermal time constant, there is no difference between continuous and intermittent ratings above a few second conduction period.

#### (a) Continuous Current Ratings.

Continuous current ratings of SCRs are normally given in terms of average or rms values depending upon whether the device is unilateral or bilateral. However, rms current rating is more commonly used in the rating procedure for a device. The rms current rating of the device is useful, because it is essentially independent of the conduction angle, whereas the average current rating decreases with the decrease in conduction angle. Also, the rms current rating of the device is larger than the average current rating. This rms current flows through the conductive part of the lead assembly, the device wiring and internal assembly parts and raises the temperature. The rms current rating must be limited to a safe value to prevent excessive heating in the resistive elements of the SCR, such as joints, leads etc. The rms current rating is also important when SCRs are used to supply large peak current to a load with low duty cycle.

#### (b) Repetitive Overload Current Ratings.

It is very common for rectifier equipment to frequently run on over-load. Though the duration of over-load is short, it is repetitive. It is quite obvious that the peak allowable junction temperature is never to be exceeded under any condition. So, the magnitude, duration and repetitive frequency of the overload current of the device should be such that under no case the peak allowable junction temperature is exceeded. This again depends on the thermal



resistance and transient thermal impedances of the device and the type and size of the heat sink. It also depends on the method of cooling (i.e. natural air cooling or forced air cooling), the velocity of cooling air, ambient temperature etc.


### (c) Non-repetitive Surge Current Ratings.

Non-repetitive surge current ratings of the SCRs are provided by the manufacturer. Such surge current is assumed to be imposed on the device when it is operating at the maximum rated voltage, current and temperature condition in a half-wave circuit delivering a resistive load. These ratings are such that during the surge current, the maximum repetitive junction temperature of the device may be exceeded. During this brief period, the forward blocking capability of the device is lost until the device is cooled down to or below the maximum rated operating temperature. The surge current is not a regular feature of the device and occurs during severe fault condition. These ratings provide the instantaneous over-load capacity of the device and are used in designing the protective devices for it. Such ratings are usually provided in terms of non-recurring surge current with respect to time duration of occurrence and  $I^2t$ . The maximum surge current rating is provided for minimum time duration of one half cycle of the supply frequency, i.e. 10 ms; for the supply frequency of 50 Hz.  $I^2t$  ratings apply for non-repetitive surge overloads shorter than one half cycle. At this condition SCR behaves like a resistor with a fixed thermal capacity. The heat dissipation during the small period is negligible.  $I^2t$  rating of the device represents the capability of the device to withstand the overload current for the specified time. The current is rms value for the time interval  $t$ .

## Over voltage and over current protection of SCR


SCRs are sensitive to **high voltage, over-current**, and any form of transients. For satisfactory and reliable operation they are required to be protected against such abnormal operating conditions. Because of complex and expensive protection, usually some margin is provided in the equipment by selecting devices with ratings higher (3 or 4 times higher) than those required for normal operation. But it is always not economical to use devices of higher ratings, hence their protection is imperative.

Over-voltage Protection.

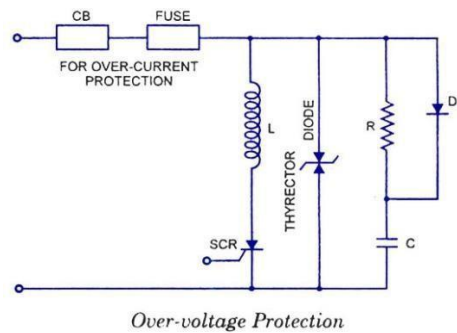

High forward voltage protection is inherent in SCRs. The SCR will breakdown and start conducting before the peak forward voltage is attained so that the high voltage is transferred to another part of the circuit (usually the load). The **turn-on of SCR** causes a large current to flow and poses a problem of over-current protection.

Over-current Protection.

 

Over-current protection can be provided by connecting a circuit breaker and a fuse in series with the SCR, as usually done for the protection of any circuit. However, there are some reservations to their use. A semiconductor device is capable of taking overloads for a limited period, so the fuse used should have high breaking capacity and rapid interruption of current. There must be a similarity of SCR and fuse  $I^2t$  rating without developing high voltage transients which endanger those SCRs in the off or infinite impedance condition. These are contradictory requirements necessitating voltage protection when fast-acting fuses are employed. Fuses when used, their arc voltages are kept below 1.5 times the peak circuit voltage. For small power applications it is pointless to employ high speed fuses for circuit protection because it may cost more than the SCR. Current magnitude detection can be employed and is used in many applications. When an over-current is detected the gate circuits are controlled either to **turn-off the appropriate SCRs**, or in phase commutation, to reduce the conduction period and so the average value of the current.

If the output to the load from the **SCR circuit** is alternating current, LC resonance provides over-current protection as well as filtering. A current limiting device employing a saturable reactor is shown in figure. With normal currents the saturable reactor  $L_1$  offers high

impedance and C and L are in series resonance to offer zero impedance to the flow of current

of the fundamental harmonic. An over-current saturates  $L_1$  and so gives negligible impedance. There is LC parallel resonance and hence infinite impedance to the flow of current at the resonant frequency.

### **dv/dt and di/dt protection of SCR**


- For reliable operation of SCR, it should be operated within the specific ratings.
- SCRs are very delicate devices and so they must be protected against abnormal operating conditions. Various protection of SCR are

di/dt Protection

dv/dt Protection
 
#### **di/dt Protection:-**

- di/dt is the rate of change of current in a device.
- When SCR is forward biased and is turned ON by the gate signal, the anode current flows.
- The anode current requires some time to spread inside the device. (Spreading of charge carriers)
- But if the rate of rise of anode current (di/dt) is greater than the spread velocity of charge carriers then local hot spots is created near the gate due to increased current density. This localised heating may damage the device.
- Local spot heating is avoided by ensuring that the conduction spreads to the whole area very rapidly. (OR) The di/dt value must be maintained below a threshold (limiting) value.
- This is done by means of connecting an inductor in series with the thyristor.




- The inductance  $L$  opposes the high di/dt variations.
- When the current variation is high, the inductor smooths it and protects the SCR from damage. (Though di/dt variation is high, the inductor 'L' smooths it because it takes some time to charge).  $L \geq [V_s / (di/dt)]$
 
#### **dv/dt Protection:-**

- dv/dt is the rate of change of voltage in SCR.

- We know that  $i_C = C \cdot dv/dt$ . ie, when  $dv/dt$  is high,  $i_C$  is high.
- This high current ( $i_C$ ) may turn ON SCR even when gate current is zero. This is called as  $dv/dt$  turn ON or false turn ON of SCR.




It is sometimes necessary to use one resistor for  $dv/dt$  and another for limiting the discharge current of the snubber capacitor. This arrangement is shown in figure (e). In this circuit,  $R_1$  and  $C_s$  are used for  $dv/dt$  protection, while  $R_1 + R_2$  is used for limiting the capacitor discharge current.

The load can also be placed in series with the snubber components as shown in figure (f).
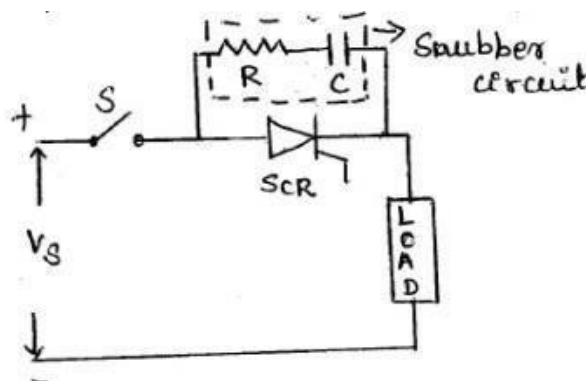
### SNUBBER CIRCUIT:-

To protect the thyristor against false turn ON or against high  $dv/dt$  a "Snubber Circuit" is used.



- The snubber Circuit is a series combination of resistor 'R' and capacitor 'C'.
- They are connected across the thyristor to be protected.
- The capacitor 'C' is used to limit the  $dv/dt$  across the SCR.
- The resistor 'R' is used to limit high discharging current through the SCR.
- When switch S is closed, the capacitor 'C' behaves as a short-circuit.
- Therefore voltage across SCR is zero.

- As time increases, voltage across 'C' increases at a slow rate.

- Therefore  $dv/dt$  across 'C' and SCR is less than maximum  $dv/dt$  rating of the device.
- The capacitor charges to full voltage  $V_s$ ; after which the gate is triggered, and SCR is turned ON and high current flows through SCR.
- As  $di/dt$  is high, it may damage the SCR. To avoid this, the resistor  $R$  in series with 'C' will limit the magnitude of  $di/dt$ .
- The technique of 'snubbing' can apply to any switching circuit, not only to thyristor/triac circuits.
- The rate of rise of turn-off voltage is determined by the time constant  $R_L C$ . Where  $R_L$  is the circuit minimum load resistance, for instance the cold resistance of a heater or lamp, the winding resistance of a motor or the primary resistance of a transformer.

### **Describe the process involved in selecting an SCR for a particular application**

The voltage and current ratings are important before selecting an SCR for a particular application. The voltage ratings of SCRs are given for both steady-state and transient operation and for both forward and reverse blocking conditions. Consideration must be given to:

- Load Voltage - AC or DC, Line Voltage.
- Load Current - AC or DC, Max and Min.
- Input Voltage - AC or DC, Max and Min.
- Ambient Temperature - Required for Derating and heatsink calculations.
- Mounting Style - PCB, Chassis or DIN Rail Mounting
- International Approvals - UL, CSA, VDE, TUV, etc.

### **Reliability of SCR and mean time between failures (MTBF)**

As a silicon semiconductor device, the SCR is compact, static, capable of being passivated and hermetically sealed, silent in operation and free from the effects of vibration and shock. A properly designed and fabricated SCR *has no inherent failure mechanism*. When properly chosen and protected, it should *have virtually an operating life without limits*, even in harsh atmosphere. Consequently, countless billions of operations can be expected, even in explosive and corrosive environments. All components — including power semiconductors — have the potential of failing or degrading in ways that could impair the proper operation of such systems. Well-known circuit techniques (including fusing and self-checking) are available to protect against the effects of such phenomena. For any systems where *safety* is in question fault analysis is recommended.

### Mean Time Between Failures (MTBF)

Calculating Mean Time Before Failure (MTBF) for a solid state relay is, at best, a tricky proposition. Unlike a typical electromechanical relay, there are several variables that will directly impact the life expectancy of a solid state relay in a given application. These variables primarily revolve around the electrical characteristics of the application, such as load current, the duty-cycle of the load, the ambient temperature inside the panel, surge currents, etc. However, mechanical issues such as the mounting method, available airflow, and thermal interface between the relay and the panel / heat sink also impact the relay's life expectancy.

Therefore, Crydom does not publish a "fixed" MTBF specification. Instead, we provide an estimated MTBF specification range based on historical observation. That is, we calculate the MTBF by taking the total in-service hours over the previous two-year period and dividing that by the number of returns we have received from the field over the same period of time (solid state relays that were misapplied by the customer are not considered in the calculation). "In-service hours" is simply calculated by taking the number of products shipped over the specified period and assuming that they were in operation for eight hours per day over a five day work week. Then, to ensure that we maintain an adequate margin of error, we assume that only 10% of all field failures are returned to us for analysis and adjust the results accordingly.

The final result yields a MTBF rating of between 2 million and 40 million hours, depending upon the product family. However, for the sake of simplicity we state that the MTBF rating for our solid state relays is >2 million hours.

**MTBF** - or Mean Time Between Failures is calculated in hrs and is a prediction of a solid state relays reliability.  $MTBF = 1/\lambda$  (failure rate)

### The three failures of an SCR (Mechanical, Electrical and Thermal)

#### Mechanical

- Auxiliary Cathode and Gate Leads not Twisted
- If the auxiliary cathode (small red) and gate (white) are not twisted together properly it can cause false triggering or the device turning on when it should be off. The proper twist for these is one twist per inch. This eliminates EMF (a.k.a. noise).
- Loose gate connection at SCR or terminal board.
- This is typically caused by improper or non-soldered gate connection to the device and/or firing board. It could also be the result of improper matching of connectors. That is,



metal or plastic undersized male connector fitting into female connector. There were incidences when they used 3/16" male with 1/4" female. This will create heat (40 volt potential), which in turn melts solder to the terminal board and breaks the connection.

- Bad snubber (R&C) network across SCR.

• Snubbers are resistor capacitor networks (circuits) which limit rapid rises in voltage or current in short time periods. If the snubber network is malfunctioning or not designed to handle the load ( as some of the older units did), spikes can be passed on to the SCR causing failure.

### **Electrical**

• Cold solder joint on either the gate drive circuit or the snubber network are suspect to poor connections. Again, it boils down to getting good connections, avoiding heat build up and making sure there are no spurious paths for the current to take.

- Bad firing amplifier.

• A SCR may show that it is not conducting when it should be. This may be caused by insufficient, or no gate drive caused by a bad firing amplifier.

- Small crack in the printed circuit board electrical circuit.

• One of the more frustrating and hard to find problems is a small crack in the printed circuit board circuitry. This shows up as an intermittent in the system and therefore is difficult to trace.

### **Thermal**

- Loss of cooling.

• The system cooling can either be liquid or air in conjunction with a pump and/or fan. If the cooling system fails, from clogged filter, loss of coolant pressure, or airflow, then the entire circuit is in danger. Significant heat is generated by these components and overheating will eventually cause junctions to start failing.

- Insufficient gate drive to the SCR.

• SCR's need a hard drive to get the total junction on and ready to accept the system current. A hard drive is typically an initial gating pulse of 25 volts at 1 amp for 1 microsecond then rapidly decaying to 3 volts and 500 milliamps. If the gate drive is insufficient to get the total junction on then when the system current pulse occurs it will hit the portion of the junction that is on. This can cause a current burn through destroying the junction thus causing a device failure.

- Cracked Insulation.

- Old insulation that has become cracked can cause a short circuit under normal operating conditions. This will cause massive failure of electronic components including the SCR.

- In summary, SCR's will not fail by themselves. Something external causes them to fail. Before you pullout the failed SCR's and install new ones make sure you locate the cause of the failure. Check the above ten possibilities. If you still don't know the reason, have the failed devices analyzed to see if the junctions will give you an indication of the failure mode.

## Chapter-8 Industrial Electronics

### Power Supplies, Stabilizers and Generation voltage regulators

#### Power Supplies

A power supply is an electronic device that supplies electric energy to an electrical load. The primary function of a power supply is to convert one form of electrical energy to another and, as a result, power supplies are sometimes referred to as electric power converters. Some power supplies are discrete, stand-alone devices, whereas others are built into larger devices along with their loads. Examples of the latter include power supplies found in desktop computers and consumer electronics devices.

Every power supply must obtain the energy it supplies to its load, as well as any energy it consumes while performing that task, from an energy source. Depending on its design, a power supply may obtain energy from various types of energy sources, including electrical energy transmission systems, energy storage devices such as a batteries and fuel cells, electromechanical systems such as generators and alternators, solar power converters, or another power supply.

All power supplies have a power input, which receives energy from the energy source, and a power output that delivers energy to the load. In most power supplies the power input and output consist of electrical connectors or hardwired circuit connections, though some power supplies employ wireless energy transfer in lieu of galvanic connections for the power input or output. Some power supplies have other types of inputs and outputs as well, for functions such as external monitoring and control.

#### Types

DC power supply

AC-to-DC supply

Linear regulator

AC power supplies

Switched-mode power supply

Programmable power supply

Uninterruptible power supply


High voltage power supply

### Generation voltage regulators

In [electrical engineering](#), particularly [power engineering](#), **voltage regulation** is a measure of change in the [voltage](#) magnitude between the sending and receiving end of a component, such as a [transmission](#) or distribution line. Voltage regulation describes the ability of a system to provide near constant voltage over a wide range of [load](#) conditions. The term may refer to a passive property that results in more or less voltage drop under various load conditions, or to the active intervention with devices for the specific purpose of adjusting voltage.

A **voltage regulator** is designed to automatically maintain a [constant voltage](#) level. A voltage regulator may be a simple "[feed-forward](#)" design or may include [negative feedback control loops](#). It may use an electromechanical [mechanism](#), or electronic components. Depending on the design, it may be used to regulate one or more [AC](#) or [DC](#) voltages.

Electronic voltage regulators are found in devices such as computer [power supplies](#) where they stabilize the DC voltages used by the processor and other elements. In automobile [alternators](#) and central [power station](#) generator plants, voltage regulators control the output of the plant. In an [electric power distribution](#) system, voltage regulators may be installed at a substation or along distribution lines so that all customers receive steady voltage independent of how much power is drawn from the line.

 

### Types

*Electronic voltage regulators*

*Electromechanical regulators*

*Automatic voltage regulator*

### Stabilizers


*It is the type of voltage regulator used as generation of voltage regulation it may be of two types A.C voltage stabilizers and D.C voltage stabilizers.*

### ***A.C voltage stabilizers***

This is an older type of regulator used in the 1920s that uses the principle of a fixed-position field coil and a second field coil that can be rotated on an axis in parallel with the fixed coil, similar to a variocoupler.

When the movable coil is positioned perpendicular to the fixed coil, the magnetic forces acting on the movable coil balance each other out and voltage output is unchanged. Rotating the coil in one direction or the other away from the center position will increase or decrease voltage in the secondary movable coil.

 This type of regulator can be automated via a servo control mechanism to advance the movable coil position in order to provide voltage increase or decrease. A braking mechanism or high ratio gearing is used to hold the rotating coil in place against the powerful magnetic forces acting on the moving coil.




### ***DC voltage stabilizers***

Many simple DC power supplies regulate the voltage using either series or shunt regulators, but most apply a voltage reference using a shunt regulator such as a Zener diode, avalanche breakdown diode, or voltage regulator tube. Each of these devices begins conducting at a specified voltage and will conduct as much current as required to hold its terminal voltage to that specified voltage by diverting excess current from a non-ideal power source to ground, often through a relatively low-value resistor to dissipate the excess energy. The power supply is designed to only supply a maximum amount of current that is within the safe operating capability of the shunt regulating device.

If the stabilizer must provide more power, the shunt regulator output is only used to provide the standard voltage reference for the electronic device, known as the voltage stabilizer. The voltage stabilizer is the electronic device, able to deliver much larger currents on demand.
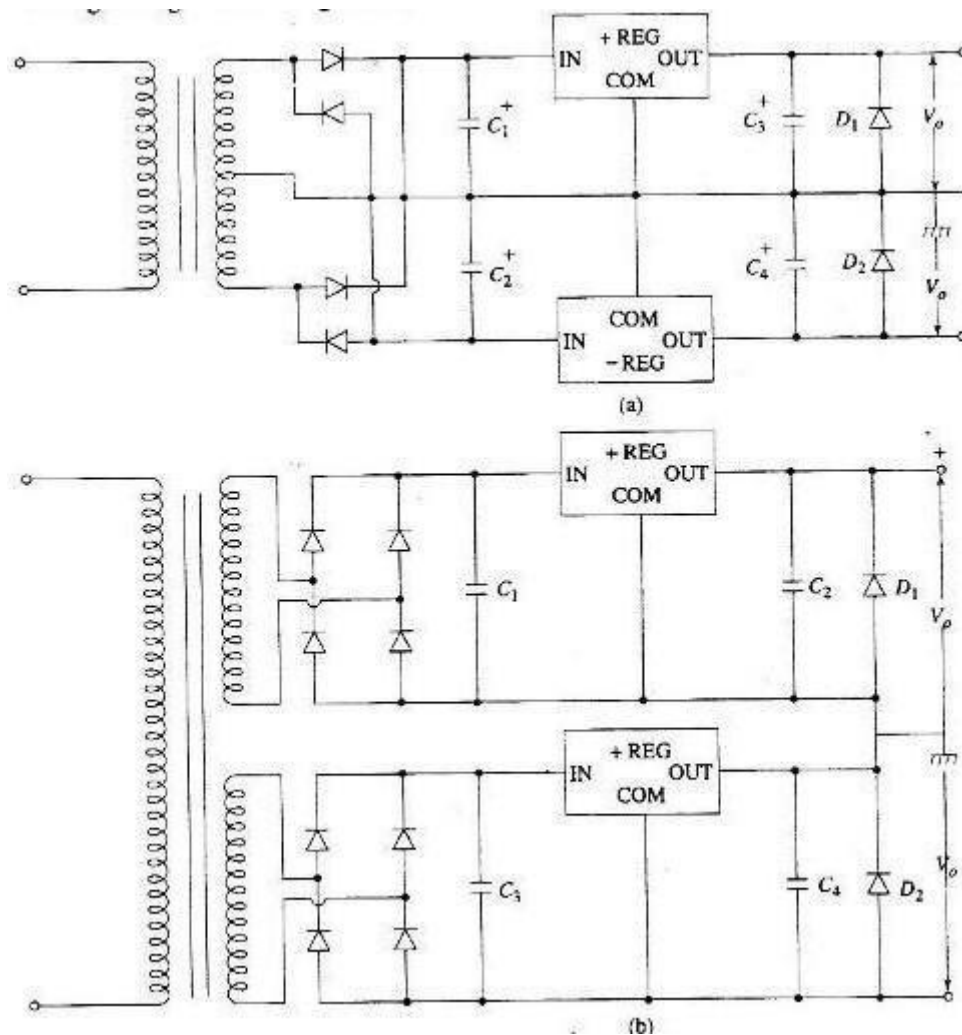
## Schematic diagram of linear power supply that provides + or – 5V and + or -15V & its operation

The simplest dual non-tracking regulator requires +ve & -ve non-regulated power supply and one three terminal +ve & -ve IC regulator. The dual unregulated DC supply may be obtained from a transformer having a centre taped secondary and two full-wave rectifiers Fig-a, a transformer having two secondary and two bridge rectifiers Fig-b.




## Schematic diagram of switched mode power supply (SMPS) and its operation & application

### SMPS (Switched Mode Power Supply)

D.C. to D.C. converters and D.C. to A.C. Converters belong to the category of **Switched Mode Power Supplies (SMPS)**. The various types of voltage regulators, used in Linear Power Supplies (LPS), fall in the category of dissipative regulator, as they have a

voltage control element usually transistor or zener diode which dissipates power equal to the voltage difference between an unregulated input voltage and a fixed supply voltage multiplied by the current flowing through it. The switching regulator acts as a continuously variable power converter and hence its efficiency is negligibly affected by the voltage difference. Hence the switching regulator is also known as ‘non-dissipative regulator’. In a SMPS, the active device that provides regulation is always operated in cut-off or in saturation mode.

The input D.C. Supply is chopped at a higher frequency around 15 to 50 kHz using an active device like the BJT, power MOSFET or SCR and the converter transformer. Here the size of the ferrite core reduces inversely with the frequency. The lower limit is around 5 kHz for silent operation and an upper limit of 50 kHz to limit the losses in the choke and in active switching elements. The transformed wave form is rectified and filtered. A sample of the output voltage is used as the feedback signal for the drive circuit for the switching transistor to achieve regulation.

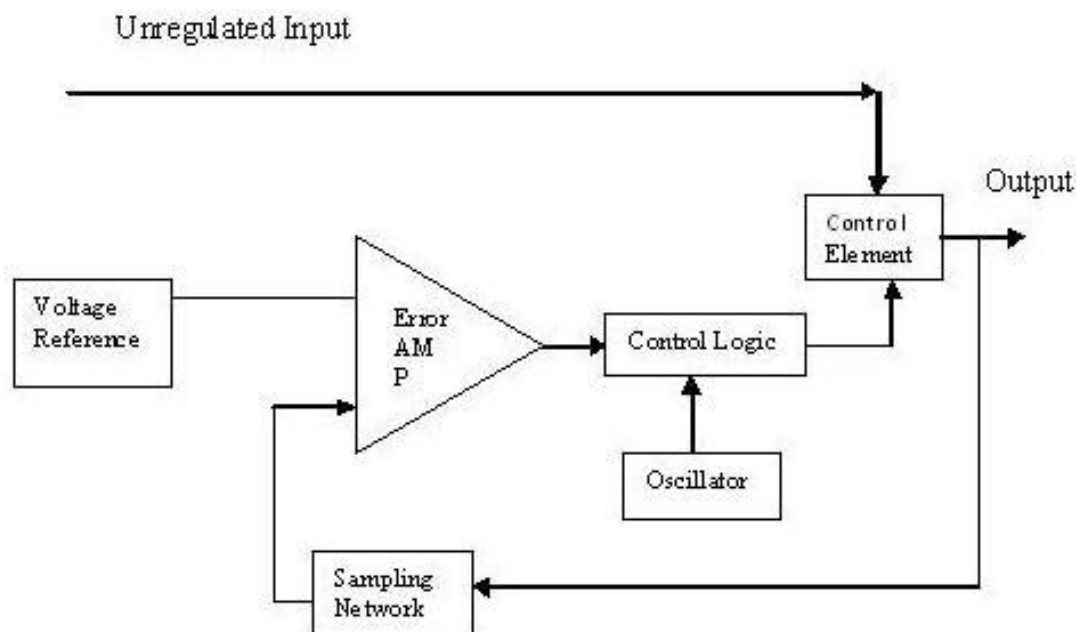


Block Diagram of Switched Mode Power Supply

The oscillator in above figure allows the control element to be switched ON and OFF. The control element usually consists of a transistor switch, an inductor, and a diode. For each switch ON, energy is pumped into the magnetic field associated with the inductor which is a transformer winding in practice. This energy is then released to the load at the desired voltage level.

By varying the duty cycle or frequency of switching, we can vary the stored energy in each cycle and thus control the output voltage. Higher efficiency is obtained since only the energy required is pumped to maintain the load current hence no power dissipation.

$$\text{Duty cycle, } \delta = \frac{T_{ON}}{T}$$

$$\text{where, } T = T_{ON} + T_{OFF}$$

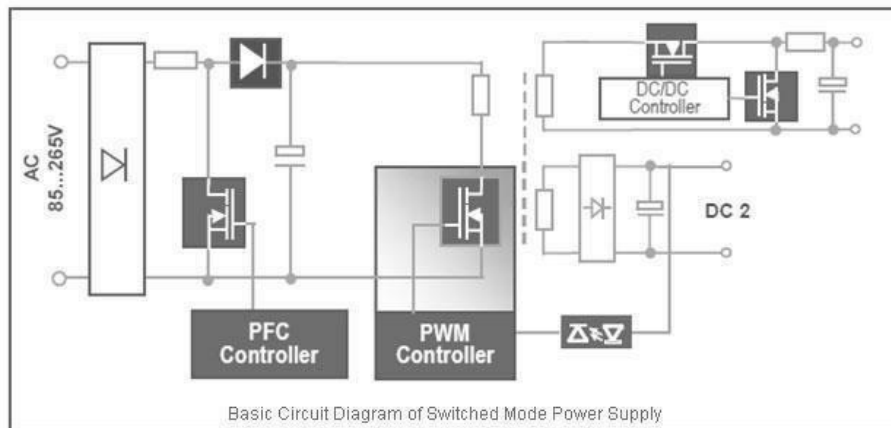

The major feature of SMPS is the elimination of physically massive power transformers and other power line magnetic. The net result is smaller, lighter package and reduced manufacturing cost, reducing primarily from the elimination of the 50 Hz components. The basic concept of switching regulator in a simple form is shown in this figure below.

### Types of SMPS:


- D.C. to D.C. Converter, Forward Converter, Flyback Converter, Self-Oscillating Flyback Converter:
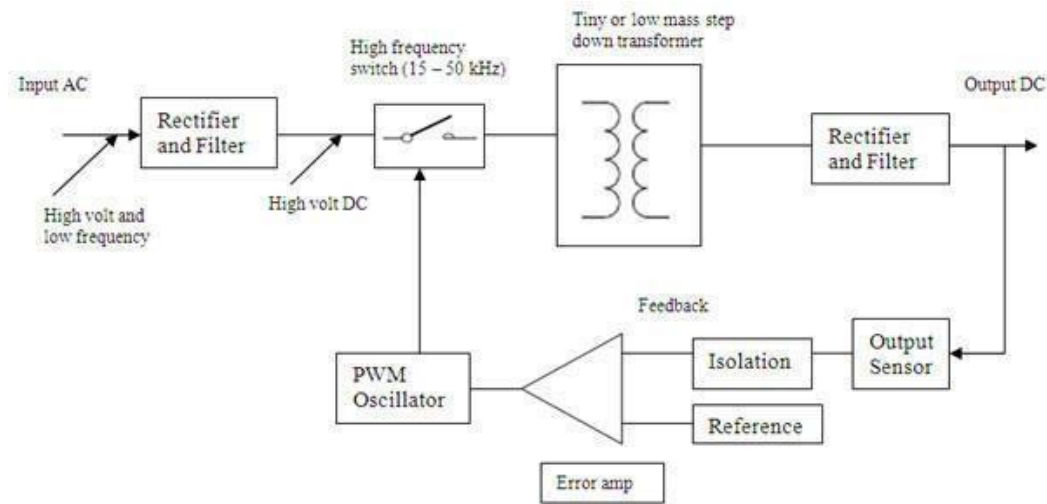
#### D.C. to D.C. Converter

Here, the primary power received from AC main is rectified and filtered as high voltage DC. It is then switched at a huge rate of speed approximately 15 kHz to 50 kHz and fed to the primary side of the step-down transformer. The step-down transformer is only a fraction of the size of a comparable 50 Hz unit thus relieving the size and weight problems. The output at the secondary side of the transformer is rectified and filtered. Then it is sent to the output of the power supply. A sample of this output is sent back to the switch to control the output voltage.



The block diagram of D.C. to D.C. converter (**SMPS**) is shown here.



SMPS rely on PWM to control the average value of the output voltage. The average value of the repetitive pulse waveform depends on the area under the waveform. As load increases, output voltage tends to fall. Most switching power supplies regulate their output using the method called Pulse – Width Modulation (PWM). The power switch which feeds the primary of the step-down transformer is driven by the PWM oscillator. When the duty cycle is at 50%, then the maximum amount of energy will be passed through the step-down transformer. As the duty cycle decreases the power transmitted is less hence low power dissipation.

The Pulse Width signal given to the switch is inversely proportional to the output voltage. The width or the ON time of the oscillator is controlled by the voltage feedback from the secondary of the rectifier output and forms a closed loop regulator. Since switching regulator is complex, modern IC packages like Motorola MC 3420/3520 or Silicon General SG 1524 can be used instead of discrete components.

### SMPS and linear power supply comparison


	LINEAR SUPPLY	SMPS
Size and weight	If a transformer is used, large due to low operating frequency (mains power frequency is at 50 or 60 Hz). Small if transformerless.	Smaller due to higher operating frequency (typically 50 kHz - 1 MHz)
Output voltage	With transformer used, any voltages available; if transformerless, not exceeding input. If unregulated, voltage varies significantly with load.	Any voltages available. Voltage varies little with load.
Efficiency, heat, and	If regulated, output voltage is regulated by dissipating excess power as heat resulting in	Output is regulated using duty cycle control, which draws

power dissipation	a typical efficiency of 30-40%; if unregulated, transformer iron and copper losses significant.	only the power required by the load. In all SMPS topologies, the transistors are always switched fully on or fully off.
Complexity	Unregulated may be diode and capacitor; regulated has a voltage regulating IC or discrete circuit and a noise filtering capacitor.	Consists of a controller IC, one or several power transistors and diodes as well as a power transformer, inductors, and filter capacitors.
Radio frequency interference	Mild high-frequency interference may be generated by AC rectifier diodes under heavy current loading, while most other supply types produce no high-frequency interference. Some mains hum induction into unshielded cables, problematical for low-signal audio.	EMI/RFI produced due to the current being switched on and off sharply. Therefore, EMI filters and RF shielding are needed to reduce the disruptive interference.

## Schematic diagram of SCR battery charger and explain
 
### Introduction to Battery Charger Using SCR:

The battery is charged with small amount of AC voltage or DC voltage. So if you want to charge your battery with AC source then should follow these steps, we need first limit the large AC voltage, need to filter the AC voltage to remove the noise, regulate and get the constant voltage and then give the resulting voltage to the battery for charging. Once charging is completed the circuit should automatically turned off.




Block Diagram of Battery Charger Using SCR

The AC source is given to the step down transformer which converts the large AC source into limited AC source, filter the AC voltage and remove the noise and then give that voltage to the SCR where it will rectify the AC and give the resulting voltage to the battery for charging.
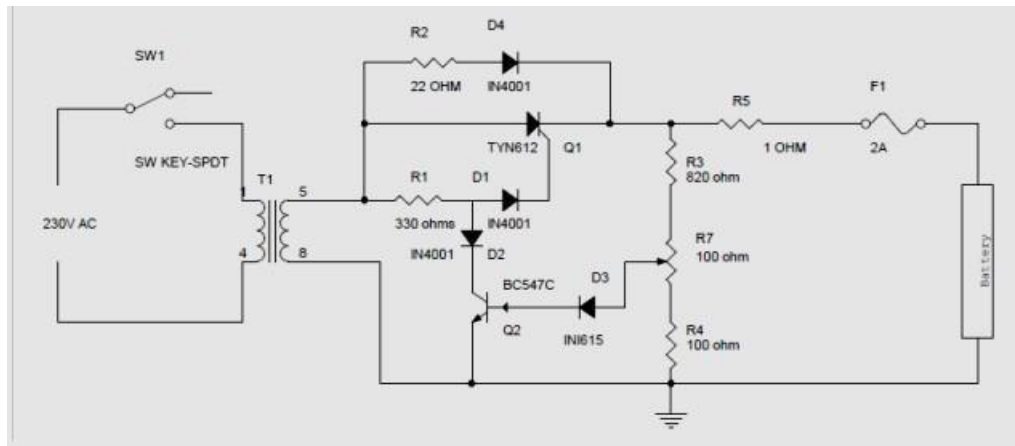
### Circuit Diagram of Battery Charger Using SCR:

Circuit diagram of the Battery Charger Circuit using SCR can be seen below:



### Circuit Diagram Explanation:


- The AC main voltage is given to the step down transformer the voltage should be down to 20V approx. the step down voltage is given to the SCR for rectification and SCR rectifies AC main voltage. This rectified voltage is used to charge battery.
- When the battery connector to the charging circuit, the battery will not be dead completely and it will get discharged this will give the forward bias voltage to the transistor through the diode D2 and resistor R7 which will get turned on. When the transistor is turned on the SCR will get off.
- When the battery voltage is dropped the forward bias will be decreased and transistor gets turned off. When the transistor is turned off automatically the diode D1 and resistor R3 will get the current to the gate of the SCR, this will triggers the SCR and gets conduct. SCR will rectifies the AC input voltage and give to the battery through Resistor R6.
- This will charge the battery when the voltage drop in the battery decreases the forward bias current also gets increased to the transistor when the battery is completely charged the Transistor Q1 will be again turned on and turned off the SCR.

### Schematic diagram of power supply using SCR for electrolytic process in industries and explain


Online UPS system and offline UPS system

Block diagram of UPS system and its operation & application
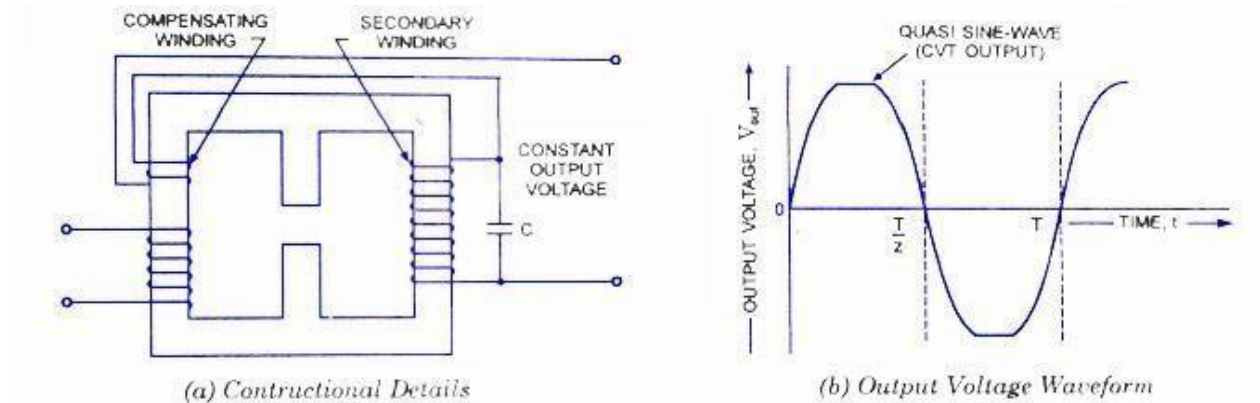
## Draw the diagram of AC servo voltage transformer (CVT) type & AC voltage stabilizer and explain its operation



With the popularisation of PCs, the constant voltage transformers (CVTs) have also become equally popular. The CVT is simply a magnetic transformer of a special construction that has a capacitor connected across the secondary winding of the transformer. In an ordinary transformer, the primary and secondary windings are wound near each other so that whenever there is a change of voltage across the primary there is a corresponding change in the secondary voltage depending upon the ratio of the turns on the two windings. However, in a CVT the primary and secondary windings are wound separately from each other, as illustrated in figure. To set up field in between the coils, a separate shunt path is provided between the two windings but an airgap is formed in the shunt path. A capacitor is connected across suitable tapings of the secondary winding. The constructional details of a CVT are shown in the figure.

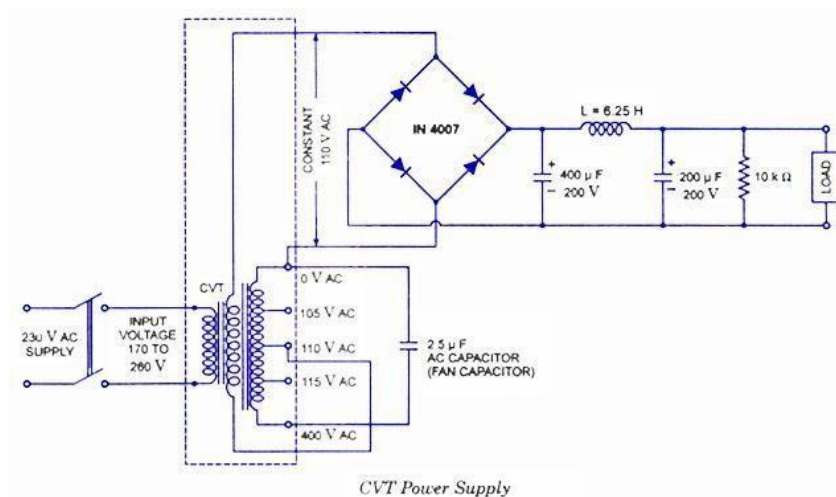

CVT Power Supply

### **Operation of CVT.**

The portion of the magnetic core over which the secondary winding is wound is saturated, while the portion over which the primary is wound is not saturated. A capacitor is connected across the secondary winding to tune out the output at a frequency very close to 50 Hz. This capacitor also makes the current in the secondary winding to increase which helps in the saturation of the secondary flux. Since the secondary ac flux is restricted to a saturated value for a large range of the input voltage (170-270 V), a constant voltage is available across the secondary winding. The output voltage will not be of a pure sinusoidal waveform but will be an approximate sinewave with the peaks flattened approaching a square wave. Output voltage waveform of a CVT is shown in figure. In figure, a compensating winding is shown connected in series to the secondary to improve the CVT performance.

If a CVT is placed at the output of a square wave inverter (in the UPS), care must be taken to control the frequency of the inverter, since the CVT is sensitive to the frequency of its input supply.

The reason we use a CVT and not a voltage stabilizer for computer applications is that in the voltage stabilizer relays are present and when these relays operate (switch), the output voltage may be interrupted for a short time. Such a transient may not be desirable for computers which may cause the computer to reboot. Also, the CVT provides a clean spike-free output voltage. The voltage regulation possible in a CVT also is good.

The input voltage ranges 170 to 260 V and output regulation is  $230 \pm 2\%$  at no load to full-load. Distortion-approximately 5% under full-load conditions. Rating of 50, 150, 250, 350, 500, 750, 1000, 2000 VA.

A practical circuit of a CVT power supply is given in figure.


### **Applications:**

The CVT's are used for various applications like computers, data processing equipment, audio/video equipment, photo processing equipment, bio-medical equipment, telex, EPABX, fax, cash registers, electronic typewriters, internet application, modem & other accessories like netphone, control panels, etc.
 
## Timer( ON & OFF delay) Circuit using IC 555 & Duty cycle.

The 555 timer IC is an integrated circuit (chip) used in a variety of timer, pulse generation, and oscillator applications. The 555 can be used to provide time delays, as an oscillator, and as a flip-flop element. Derivatives provide up to four timing circuits in one package.

This circuit 555 to the IC number on the circuit Mono Stable. Multi Vibrator. or Delay circuit with operating environment that provides a second output level be The voltage is low (logic -0") and high-level voltage (logic -1"). When you click the switch S1 pin 2 of the IC will be shot down ground. The motive for the IC1 with low voltage (logic -0"). Resulting in the output pin 3 of IC voltage levels at higher or equivalent supply. it making light LED1. Experience in the scheduling itself. And in setting up or slow down time depends on the R2, C1.And VR1 to adjust the scheduling easier.



### Modes


The 555 has three operating modes:

- **Monostable mode:** In this mode, the 555 functions as a "one-shot" pulse generator. Applications include timers, missing pulse detection, bouncefree switches, touch switches, frequency divider, capacitance measurement, pulse-width modulation (PWM) and so on.
- **Astable (free-running) mode:** The 555 can operate as an oscillator. Uses include LED and lamp flashers, pulse generation, logic clocks, tone generation, security alarms, pulse position modulation and so on. The 555 can be used as a simple ADC, converting an analog value to a pulse length. E.g. selecting a thermistor as timing resistor allows the use of the 555


in a temperature sensor: the period of the output pulse is determined by the temperature. The use of a microprocessor based circuit can then convert the pulse period to temperature, linearize it and even provide calibration means.

- Bistable mode or Schmitt trigger: The 555 can operate as a flip-flop, if the DIS pin is not connected and no capacitor is used. Uses include bounce-free latched switches.

#### Monostable

 

Schematic of a 555 in monostable mode

 

The relationships of the trigger signal, the voltage on C and the pulse width in monostable mode

In the monostable mode, the 555 timer acts as a "one-shot" pulse generator. The pulse begins when the 555 timer receives a signal at the trigger input that falls below a third of the voltage supply. The width of the output pulse is determined by the time constant of an RC network, which consists of a capacitor (C) and a resistor (R). The output pulse ends when the voltage on the capacitor equals  $2/3$  of the supply voltage. The output pulse width can be lengthened or shortened to the need of the specific application by adjusting the values of R and C.[5]


The output pulse width of time  $t$ , which is the time it takes to charge  $C$  to  $2/3$  of the supply voltage, is given by

$$t = RC \ln(3) \approx 1.1RC$$

where  $t$  is in seconds,  $R$  is in ohms (resistance) and  $C$  is in farads (capacitance).

While using the timer IC in monostable mode, the main disadvantage is that the time span between any two triggering pulses must be greater than the  $RC$  time constant.[6]


#### Bistable

 

Schematic of a 555 in bistable mode

In bistable (also called Schmitt trigger) mode, the 555 timer acts as a basic flip-flop. The trigger and reset inputs (pins 2 and 4 respectively on a 555) are held high via Pull-up resistors while the threshold input (pin 6) is simply floating. Thus configured, pulling the trigger momentarily to ground acts as a 'set' and transitions the output pin (pin 3) to  $V_{cc}$  (high state). Pulling the reset input to ground acts as a 'reset' and transitions the output pin to ground (low state). No timing capacitors are required in a bistable configuration. Pin 5 (control voltage) is connected to ground via a small-value capacitor (usually 0.01 to 0.1  $\mu F$ ); pin 7 (discharge) is left floating.[7]
 
#### Astable (Standard 555 astable circuit)





In astable mode, the 555 timer puts out a continuous stream of rectangular pulses having a specified frequency. Resistor R1 is connected between VCC and the discharge pin (pin 7) and another resistor (R2) is connected between the discharge pin (pin 7), and the trigger (pin 2) and threshold (pin 6) pins that share a common node. Hence the capacitor is charged through R1 and R2, and discharged only through R2, since pin 7 has low impedanceto ground during output low intervals of the cycle, therefore discharging the capacitor.

In the astable mode, the frequency of the pulse stream depends on the values of R1, R2 and C:

$$f = \frac{1}{\ln(2) \cdot C \cdot (R_1 + 2R_2)} [8]$$

The high time from each pulse is given by:

$$\text{high} = \ln(2) \cdot (R_1 + R_2) \cdot C$$

and the low time from each pulse is given by:

$$\text{low} = \ln(2) \cdot R_2 \cdot C$$

where R1 and R2 are the values of the resistors in ohms and C is the value of the capacitor in farads.

The power capability of R1 must be greater than.  $\frac{V_{cc}^2}{D}$

Particularly with bipolar 555s, low values of  $R_1$  must be avoided so that the output stays saturated near zero volts during discharge, as assumed by the above equation. Otherwise the output low time will be greater than calculated above. The first cycle will take appreciably longer than the calculated time, as the capacitor must charge from 0V to 2/3 of VCC from power-up, but only from 1/3 of VCC to 2/3 of VCC on subsequent cycles.

To achieve a duty cycle of less than 50% a small diode (that is fast enough for the application) can be placed in parallel with R2, with the cathode on the capacitor side. This bypasses R2 during the high part of the cycle so that the high interval depends approximately only on R1 and C. The presence of the diode is a voltage drop that slows charging on the capacitor so that the high time is longer than the expected and often-cited  $\ln(2) \cdot R_1 C = 0.693 R_1 C$ . The low time will be the same as without the diode as shown above. With a diode, the high time is

$$\text{high} = R_1 C \cdot \ln \left( \frac{2V_{cc} - 3V_{\text{diode}}}{V_{cc} - 3V_{\text{diode}}} \right)$$


where  $V_{diode}$  is when the diode has a current of  $1/2$  of  $V_{cc}/R1$  which can be determined from its datasheet or by testing. As an extreme example, when  $V_{cc}= 5$  and  $V_{diode}= 0.7$ , high time =  $1.00 R1C$  which is 45% longer than the "expected"  $0.693 R1C$ . At the other extreme, when  $V_{cc}= 15$  and  $V_{diode}= 0.3$ , the high time =  $0.725 R1C$  which is closer to the expected  $0.693 R1C$ . The equation reduces to the expected  $0.693 R1C$  if  $V_{diode}= 0$ .

The operation of RESET in this mode is not well defined, some manufacturers' parts will hold the output state to what it was when RESET is taken low, others will send the output either high or low.

## Chapter-9. Applications
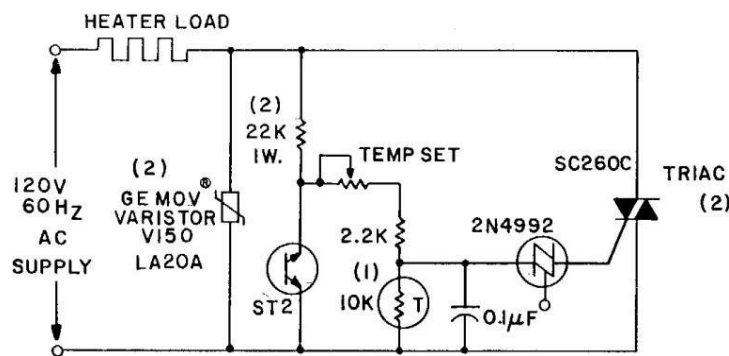
### 9.1 Temperature controlled circuit with thermistor and TRIAC

The circuit can control up to 6 kW of heating, with moderate gain, using a 25-amp triac (SC260D). Feedback is provided by the negative temperature co-efficient (NTC) thermistor, which is mounted adjacent to the environment being temperature controlled. The temperature set potentiometer is initially adjusted to the desired heating level. As the thermistor becomes heated by the load, its resistance drops, phasing back the conduction angle of the triac, so the load voltage is reduced.



(Circuit diagram of Temperature controller)

The ST2 diac is used as a back-to-back zener diode. Its negative resistance region in its E-I characteristic provides a degree of line voltage stabilization. As the input line voltage increases, the diac triggers earlier in the cycle and, hence, the average charging voltage to the 0.1  $\mu$ F capacitor, decreases.


### Simple Burglar Alarm Circuit

#### Description

Here is a simple but effective burglar alarm circuit that can be fixed on windows to detect break through. The circuit uses a fine wire element fixed as a network through the window glass for sensing the break through. Normally the base of Q1 is held to ground potential by the wire element. So Q1 will be off and SCR H1 will not be conducting, and horn will be off. When the wire element is broken the base of Q1 will be raised to positive potential, Q1 will be on and so SCR H1 (TYN 612) will be ON making the horn to blow and

this condition will be latched by the SCR. The circuit remains ON until the normal condition is restored or the power supply is switched OFF.
 
### Burglar Alarm Circuit Diagram with Parts List .



(Burglar Alarm Circuit Diagram)

- To make the window foil make a loop of very fine wire through the window glass (two or three lines running in both direction is enough). See figure. Connect the two free ends of the wires to point A & B as shown in circuit diagram.
- To setup the circuit, make S1 open and adjust R2 to get a 1V between base of Q1 and ground. (0.7 V is enough to ON Q1). Now transistor will be ON and horn will be blowing.
- Now, close S1 and reset the power supply. The transistor Q1 will be off and horn will not be blowing. The circuit is ready

## Fire alarm circuit and explain


### Description.

Here is a simple fire alarm circuit based on a **Light Dependent Resistor (LDR)** and lamp pair for sensing the fire. The alarm works by sensing the smoke produced during fire. The circuit produces an audible alarm when the fire breaks out with smoke.

When there is no smoke the light from the bulb will be directly falling on the LDR. The LDR resistance will be low and so the voltage across it (below 0.6V). The transistor will be OFF and nothing happens. When there is sufficient smoke to mask the light from falling on LDR, the LDR resistance increases and so do the voltage across it. Now the transistor will switch to ON. This gives power to the IC1 and it outputs 5V. This powers the tone generator IC UM66 (IC2) to play a music. This music will be amplified by IC3 (TDA 2002) to drive the

speaker. Resistor R6 is meant for protecting the transistor when R4 is turned towards low resistance values. Resistor R2 and R1 forms a feedback network for the TDA2002 and C1 couples the feed back signal from the junction of R1 & R2 to the inverting input of the same IC.

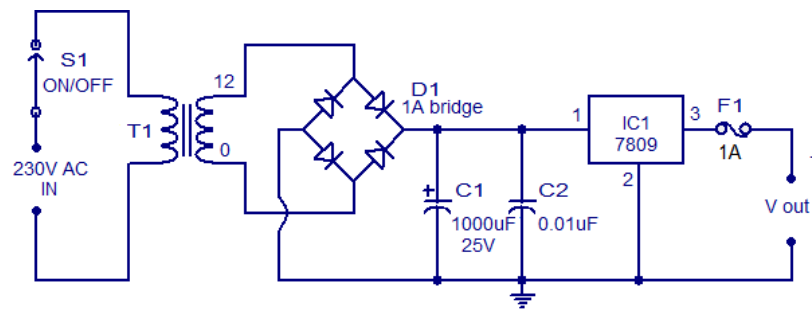The diode D1 and D2 in combination drops 1.4 V to give the rated voltage (3.5V ) to UM66. UM66 cannot withstand more than 4V.



(circuit diagram of Fire alarm)

A well regulated power supply is essential for this circuit because even slight variations in the supply voltage could alter the biasing of the transistor used in the fire sensing section and this could seriously affect the circuit's performance.


A regulated 9V/500mA power supply that can be used for powering the basic fire alarm circuit and its modified versions is shown above. Transformer T1 is a 230V primary, 12V secondary, 500mA step down transformer. D1 is a 1A bridge which performs the job of rectification. Capacitor C1 filters the rectifier output and C2 is the AC by-pass capacitor. IC1 (7809) is a 9V fixed positive voltage regulator. The output of the rectifier+filter section is connected to the input of 7805 and a regulated steady 9V is obtained at its output. S1 is the ON/OFF switch. F1 is a 500mA safety fuse.

## Smoke detector circuit and operation

Relies on the smoke that is produced in the event of a fire and passes between a bulb and an LDR, the amount of light falling on the LDR decreases. This type of circuit is called optical smoke detector.

This causes the resistance of LDR to increase and the voltage at the base of the transistor is pulled high due to which the supply to the COB (chip-on-board) is completed. The sensitivity of the *smoke detector* depends on the distance between bulb and LDR as well as

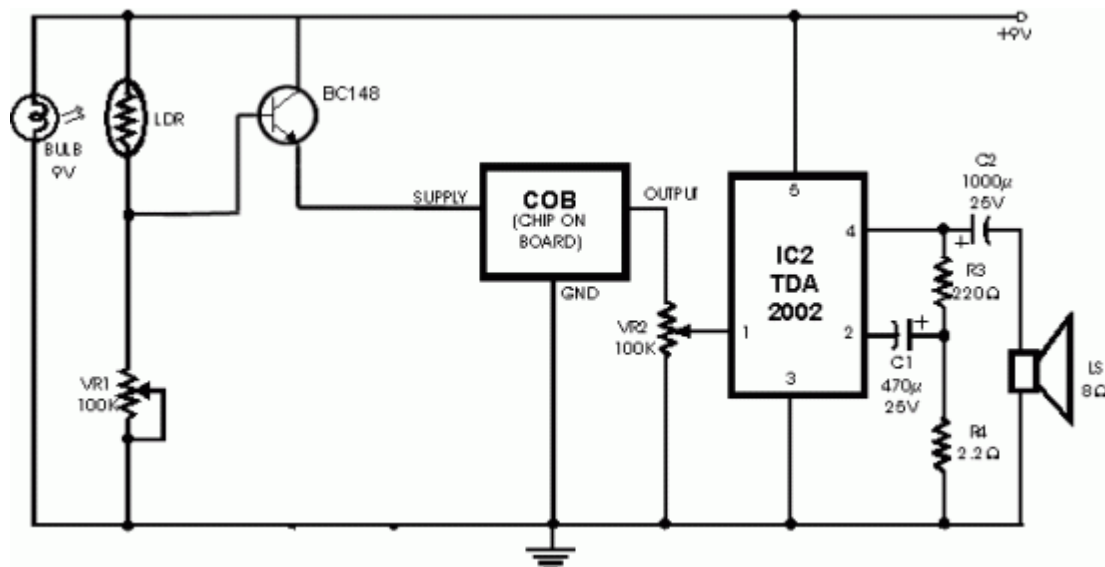setting of preset VR1. Thus by placing the bulb and the LDR at appropriate distances, one may vary preset VR1 to get optimum sensitivity.



(Circuit diagram of Smoke detector)


## Proximity alarm circuit

This presence detector or proximity sensor circuit reacts in presence of any conductor object including humans. Sensitivity is adjustable with P1 which will be located at a great distance from the rest of the presence detector circuit. This circuit does not detect object movement but can act as an proximity sensor!

The sensitivity of the proximity sensor circuit can be adjusted with P1 for the desired distance. One of its obvious uses is to open a door automatically. For this the sensor must be placed on the front of the door.

The presence detector is made of one oscillator with T1 and a monostable. The oscillator is a Clapp one, well known for its frequency stability. The surface of the sensor acts as a capacitor for the oscillator circuit and in this configuration the frequency is around 1MHz.

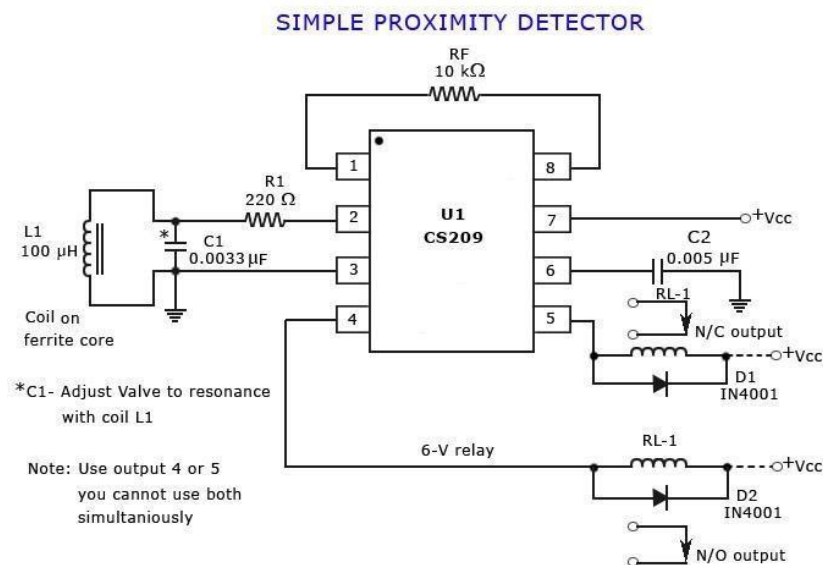The switching time can be adjusted with P2. Do not bring metallic objects in the proximity of the circuit because if doing so the relay will stay closed! This circuit can be used as a detector of aggressive liquids, the advantage being that the surface of the sensor will not come in contact with the liquid.



(Circuit diagram of Proximity detector)


## Flame failure device (flame out monitor circuit)

A minimum amount of hardware is needed to build a simple flame or fire failure monitor that enables you to monitor the status of the flame in a chamber/furnace. Owing to its integrated alarm generator, the interface can be easily adapted for use with a wide range of light/heat sensors. Here a readily available photo transistor 2N5777 (T1) works as the flame sensor. The 5V regulated dc supply for this circuit can be derived from a 12 V mains adaptor or a 9V rechargeable battery.

In the presence of the flame, T1 conducts (resistance low) and most of the base current of relay driver transistor T2 find an alternative easy path via T1. As a result T2 remains cutoff. If flame is absent, T1 behaves almost an open circuit, and the current through P1 and R1 flows into the transistor's (T2) base.

Next, the 5V reed relay is energised and 5V positive supply is extended to the alarm generator circuit built around the siren generator UM3561(IC1). Output signals from IC1 is amplified by transistor T2 to drive a standard 64 Ohm 1W mylar speaker.

 For optimum performance, enclose phototransistor (T1) in a suitable long tube and add an optical assembly (see fig.2). The adjustment of sensitivity set preset pot P1 is also very critical.



(Circuit diagram of flame failure device)

## Edge resistor control circuit

Current measurement (i.e., monitoring current flow into and out of electronic circuits) is an essential skill for a designer and necessary in a wide range of applications. Examples of applications include overcurrent protection, 4–20mA systems, battery chargers, high-brightness LED control, GSM base station power supply, and H-bridge motor control for which you must know the ratio of current flow into and out of a rechargeable battery (that is, the gauge function).

As more applications have become portable, demand has increased for dedicated current monitors that accomplish their task in a small package and with low quiescent current. The following discussion covers low-side and high-side current monitors and includes their architectures and applications.

Most current-measurement applications employ either the low-side principle, in which the sense resistor connects in series with the ground path (Figure 1), or the high-side principle, in which it connects in series with the hot wire (Figure 2). These two approaches pose a trade-off in different areas. The low-side resistor adds undesirable extraneous resistance in the ground path. However, the circuitry associated with the high-side resistor must cope with relatively large common-mode signals. Moreover, if the op amp in Figure 1 has its GND pin referred to the positive side of RSENSE, then its common-mode input range must extend below zero, that is, to  $\text{GND} - (\text{RSENSE} \times \text{ILOAD})$ .



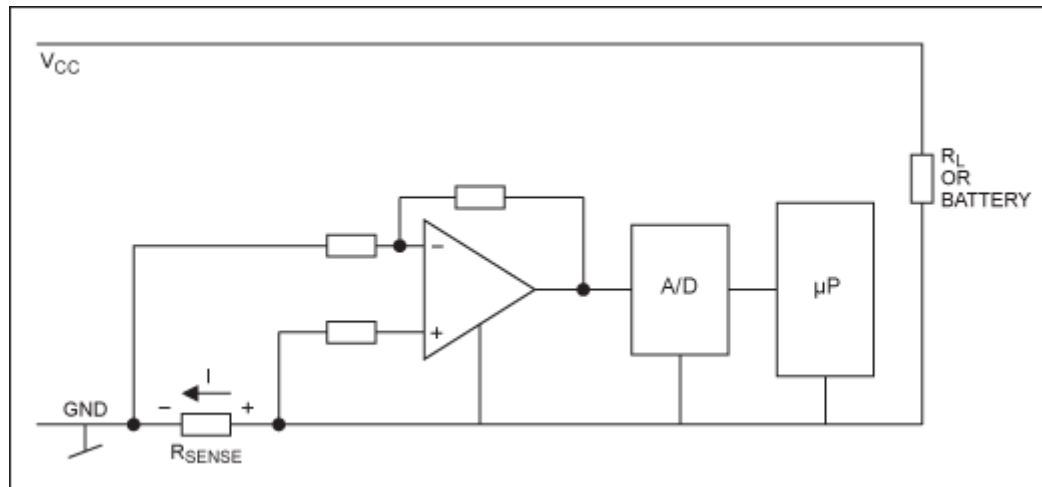


Figure 1. Principle of the low-side current monitor.

 


Figure 2. Example of a high-side current monitor.

## Optocoupler devices and application

An optocoupler (or an optoelectronic coupler) is basically an interface between two circuits which operate at (usually) different voltage levels. The key advantage of an optocoupler is the electrical isolation between the input and output circuits. With an optocoupler, the only contact between the input and the output is a beam of light. Because of this it is possible to have an insulation resistance between the two circuits in the thousands of megohms. Isolation like this is useful in high voltage applications where the potentials of two circuits may differ by several thousand volts.


The most common industrial use of the optocouplers (or optically-coupled isolators) is

as a signal converter between high-voltage pitot devices (limit switches etc.) and low voltage


solid-state logic circuits. Optical isolators can be employed in any situation where a signal must be passed between two circuits which are isolated from each other. Complete electrical isolation between two circuits (i.e. the two circuits have no conductors in common) is often necessary to prevent noise generated in one circuit from being passed to the other circuit. This is especially necessary for the coupling between high-voltage information-gathering circuits and low-voltage digital logic circuits. The information circuits are almost badly exposed to noise sources and the logic circuits cannot tolerate noise signals.

The optocouplers works well on either ac or dc high-voltage signals. For this reason, signal converters employing optical coupling are sometimes referred to the *universal* signal converters.

 The opto-coupler is a device that contains an infra-red LED and a photodetector (such as a photodiode, phototransistor, Darlington pair, SCR or triac) combined in one package. The figure of opto- coupler is given below



### Types of Optocouplers:

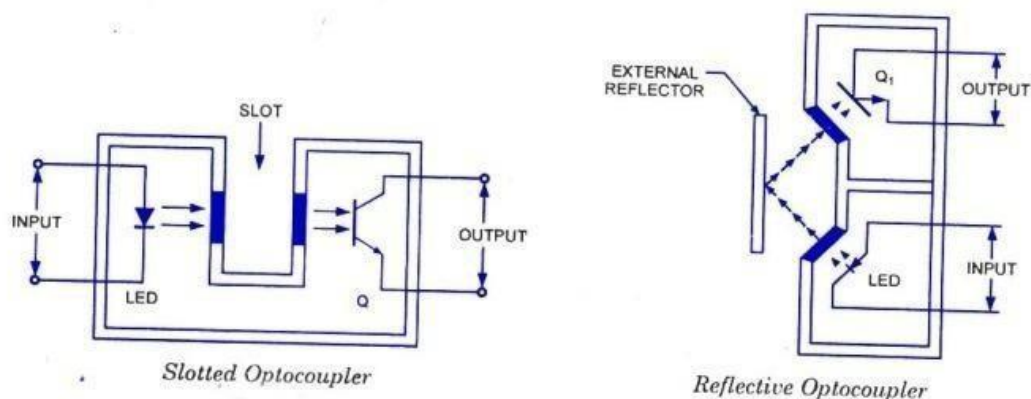

**1. Slotted Optocoupler** - A *slotted optocoupler* has a slot moulded into the package between the LED light source and the phototransistor light sensor; the slot houses transparent

windows, so that the LED light can normally freely reach the face of transistor , but can be interrupted or blocked via opaque object placed within the slot. The slotted optocoupler can


thus be employed in a variety of presence detecting applications, including end-of-tape detection, limit switching, and liquid level detection.

**2. Reflective Optocoupler** - Here the LED and phototransistor are optically screened from each other within the package, and both face outwards (in same direction) from the package. The construction is such that an optocoupled link can be set up by a reflective object (such as metallic paint or tape, or even smoke particles) placed a short distance outside the package, in line with both the LED. The reflective coupler can thus be employed in applications such as tape-position detection, engine-shaft revolution counting or speed measurement, or smoke or fog detection etc.
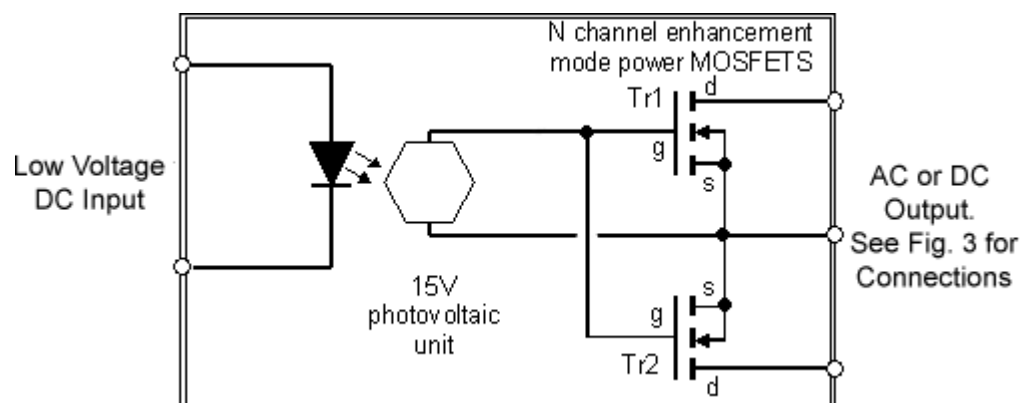
## Solid State Relays.

Solid state relay is similar to the opto coupled devices already mentioned, but using power MOSFET transistors as the switching device. Solid State Relays (SSRs) can replace many types of low power electromechanical relays.

It uses opto-coupling to provide complete electrical isolation between its low power input circuit and its high power output circuit. When the output switch is "open" (MOSFETs off) it has a nearly infinite resistance, and a very low resistance when "closed" (MOSFETs conducting heavily). It can also be used to switch either AC or DC currents.



(A typical circuit of an SSR is shown in Figure . )

A current of about 20mA through the LED is sufficient to switch on the output MOSFETS. The (infra red) light from the LED falls on the Photovoltaic unit) which comprises 25 silicon diodes. Each diode produces 0.6V to give the 15V gate potential needed to turn on the MOSFETS. Figure 2 represents a basic example of a SSR, in this case the Siemens LH1540T

**Advantages**

- Slimmer profile, allowing tighter packing.
- Totally silent operation
- SSRs are faster than electromechanical relays; their switching time is dependent on the time needed to power the LED on and off, of the order of microseconds to milliseconds
- Increased lifetime, even it is activated many times, as there are no moving parts to wear and no contacts to pit or build up carbon
- Output resistance remains constant regardless of amount of use